

# **ECE/CS 250**

## **Computer Architecture**

**Summer 2019**

### Basics of Logic Design: Finite State Machines


Tyler Bletsch  
Duke University

Slides are derived from work by  
Daniel J. Sorin (Duke), Drew Hilton (Duke), Alvy Lebeck (Duke), Amir Roth  
(Penn)


# Finite State Machine (FSM)

- FSM = States + Transitions
  - Next state = function (current state, inputs)
  - Outputs = function (current state, inputs)
- What you do depends on what state you're in
  - Think of a calculator ... if you type "+3=", the result depends on what you did before, i.e., the state of the calculator
- Canonical Example: Combination Lock
  - Must enter 3 8 4 to unlock

# How FSMs are represented

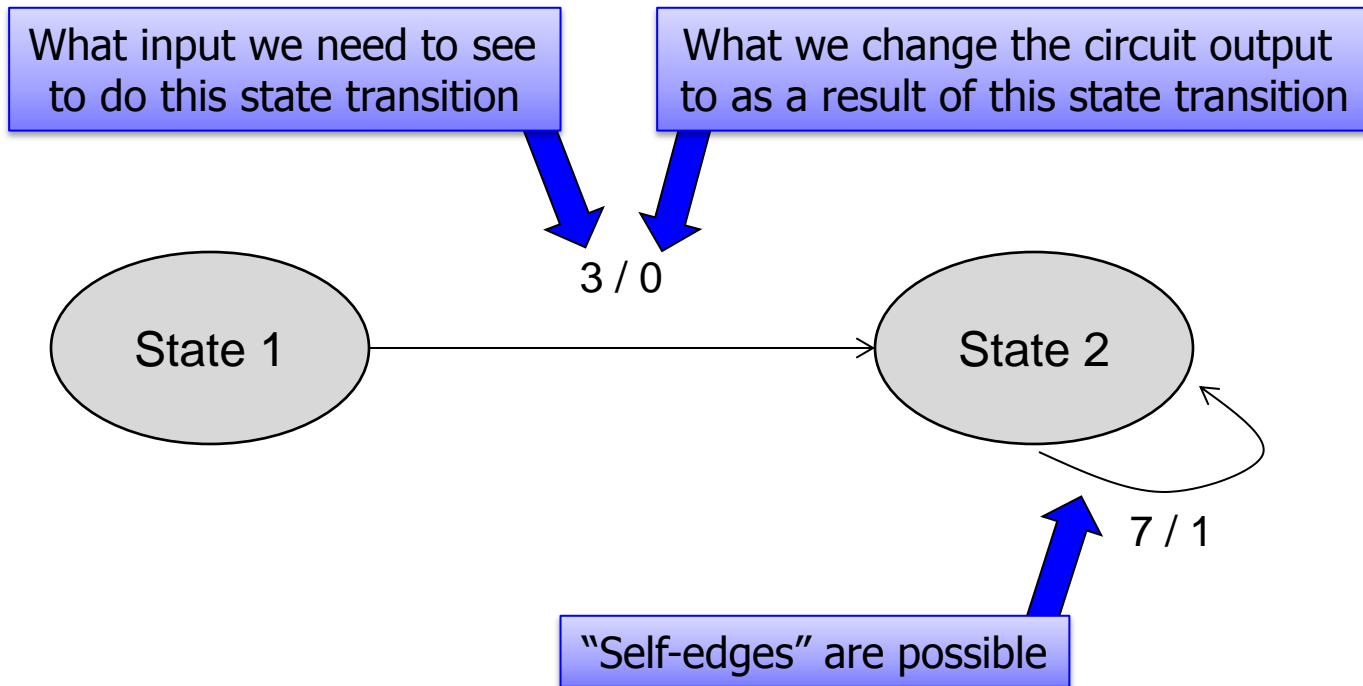


# Finite State Machines: Example

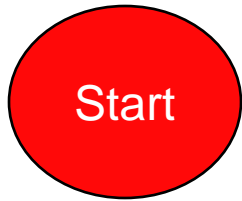


- Combination Lock Example:
  - Need to enter 3 8 4 to unlock
- Initial State called "start": no valid piece of combo seen
  - All FSMs get reset to their start state

# Finite State Machines: Example

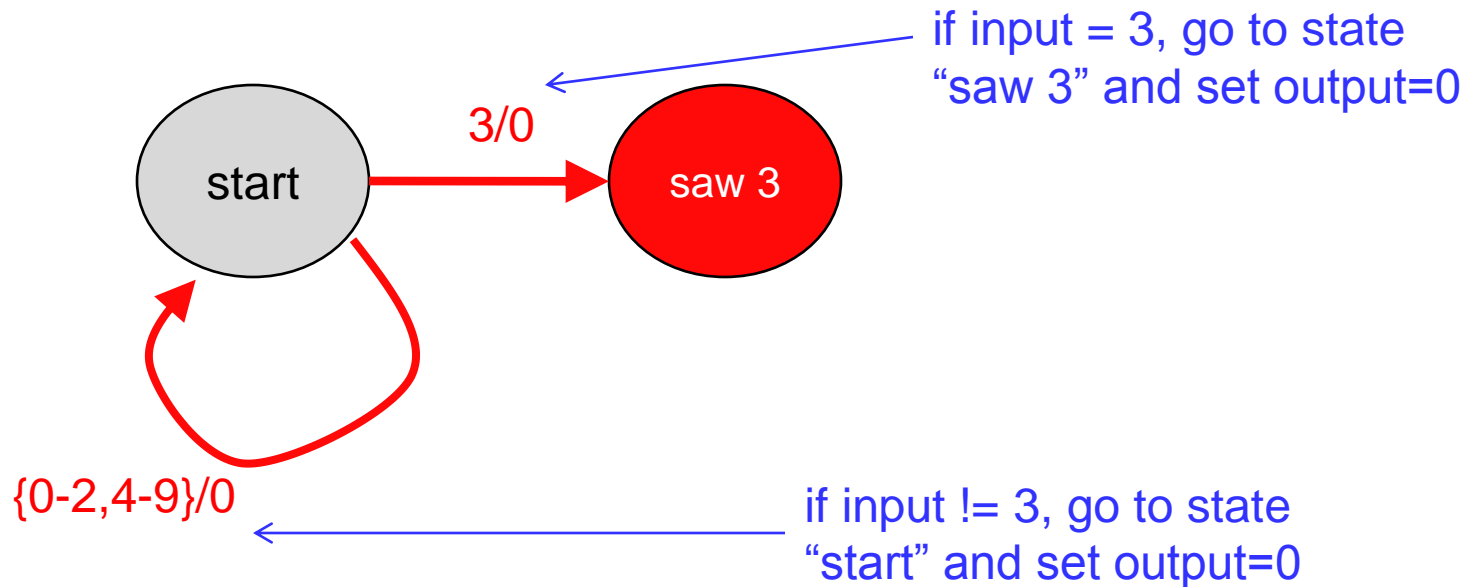


- Combination Lock Example:
  - Need to enter **3** 8 4 to unlock
- Input of 3: transition to new state, output=0
- Any other input: stay in same state, output=0

# Finite State Machines: Example

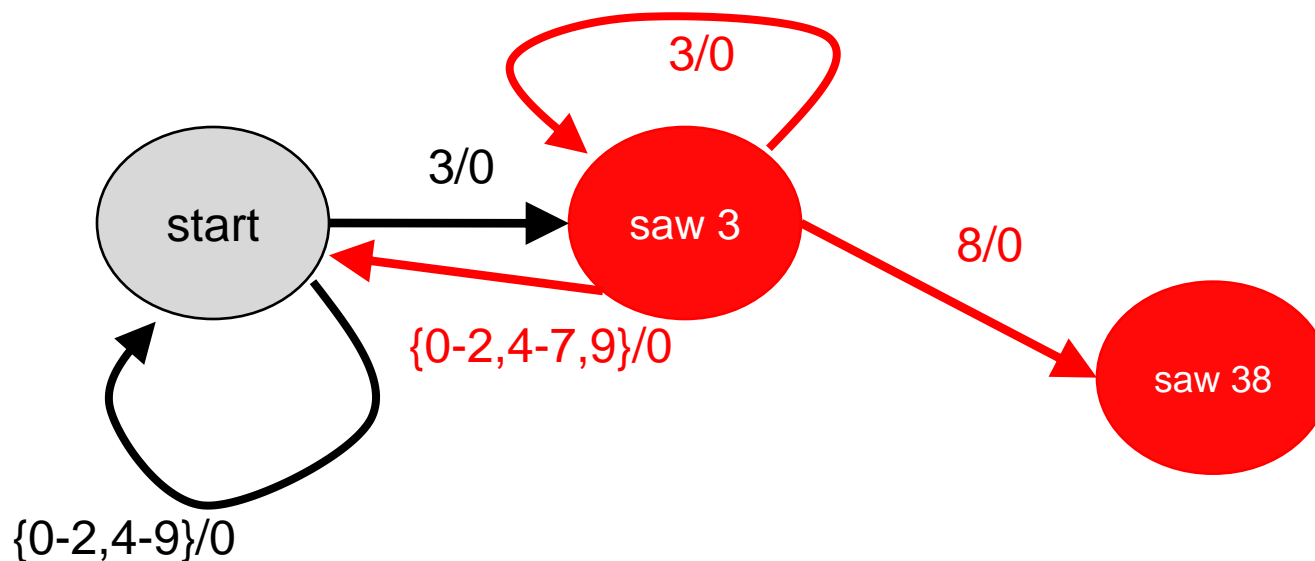


- Combination Lock Example:
  - Need to enter **3 8** 4 to unlock
- If in state "saw 3":
  - Input = 8? Goto state "saw 38" and output=0

# Finite State Machines: Example

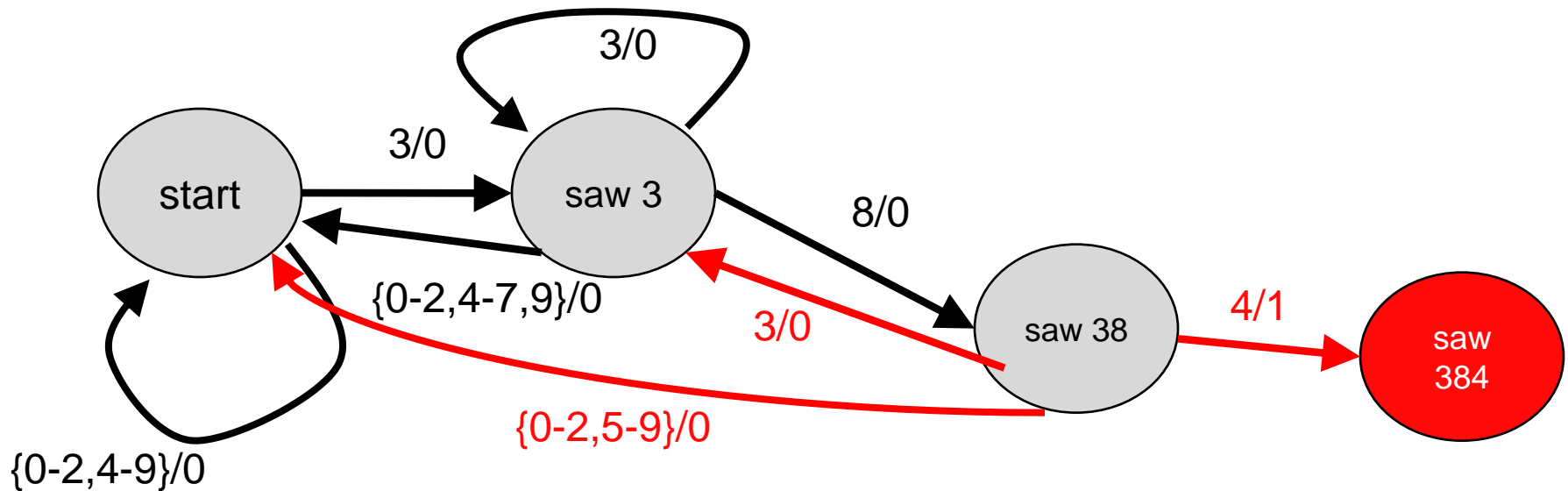

- Combination Lock Example:
  - Need to enter **3 8 4** to unlock
- If in state "saw 38":
  - Input = 4? Goto state "saw 384" and set output=1 → Unlock!


# Finite State Machines: Example

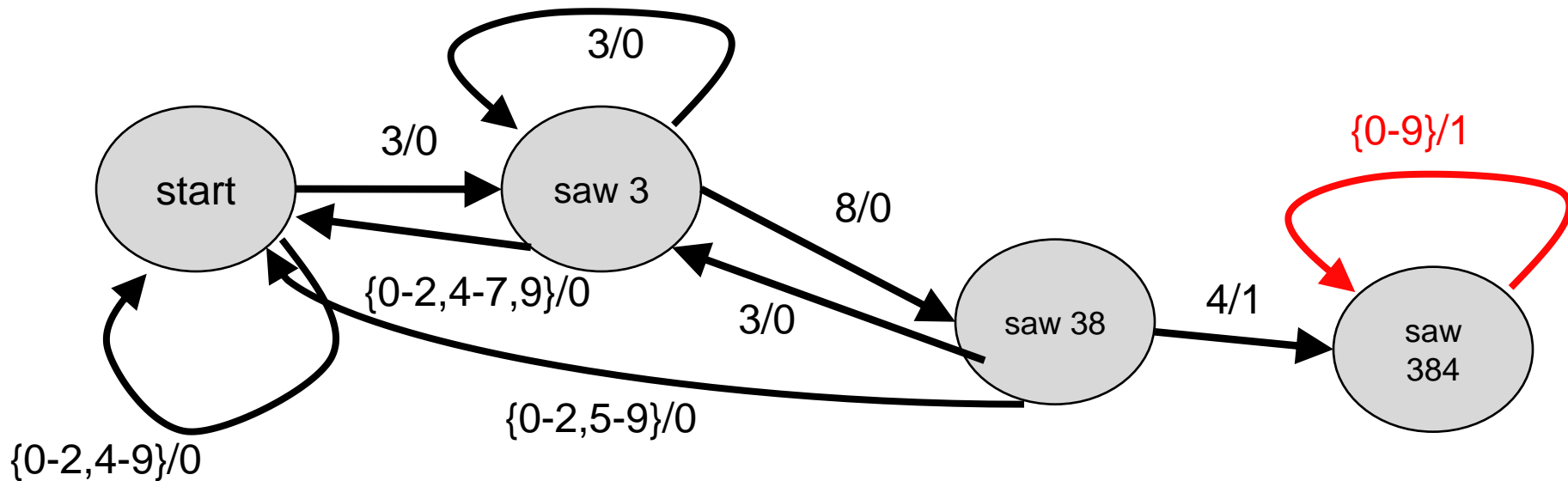

- Combination Lock Example:
  - Need to enter **3 8 4** to unlock
- If in state "saw 384":
  - Stay in this state forever and output=1



# Finite State Machines: Example

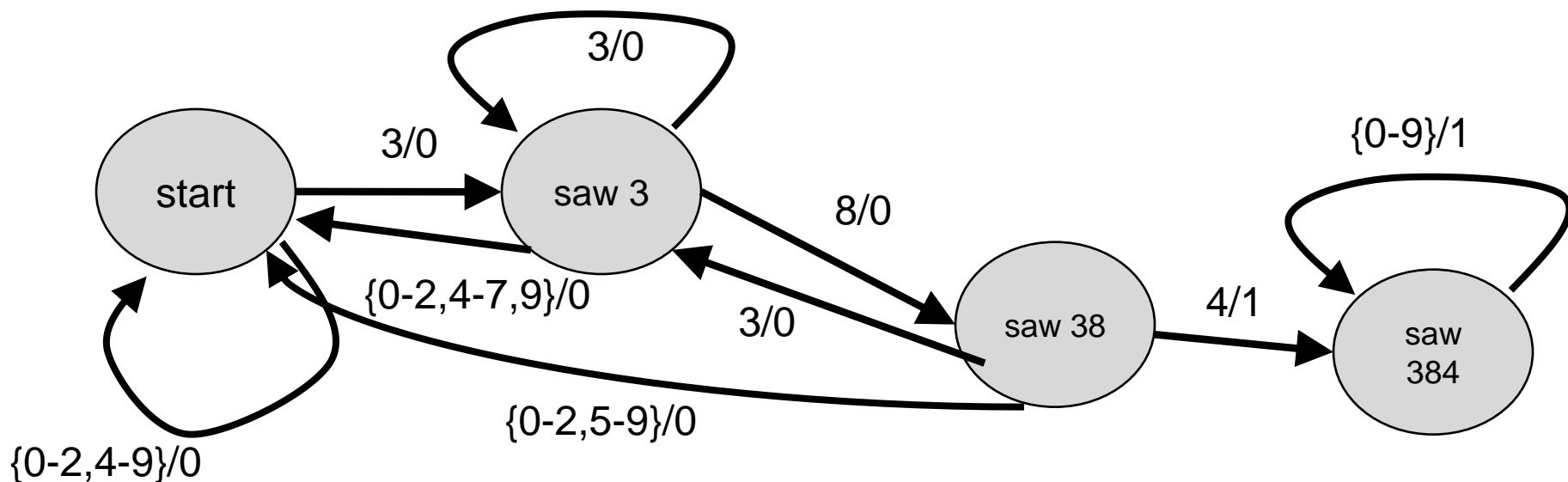

In this picture, the circles are **states**.

The arcs between the states are **transitions**.

The figure is a **state transition diagram**, and it's the first thing you make when designing a finite state machine (FSM).

# Finite State Machines: Caveats

Do NOT assume all FSMs are like this one!


- A finite state machine (FSM) has at least two states, but can have many, many more. There's nothing sacred about 4 states (as in this example). Design your FSMs to have the appropriate number of states for the problem they're solving.
  - Question: how many states would we need to detect sequence 384384?
- Most FSMs don't have state from which they can't escape.
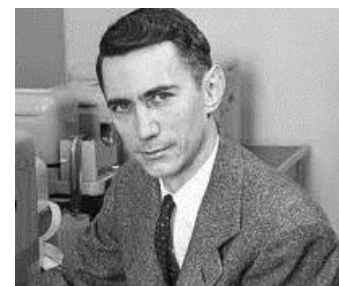
# FSM Types: Moore and Mealy

- Recall: FSM = States + Transitions
  - Next state = function (current state, inputs)
  - **Outputs = function (current state, inputs)**
  - Write the output on the edges
  - This is the most general case
    - Called a “Mealy Machine”
    - We will assume Mealy Machines in this lecture
- A more restrictive FSM type is a “Moore Machine”
  - **Outputs = function (current state)**
  - Write the output in the states
  - More often seen in software implementations





“Mealy Machine”  
developed in 1955  
by George H. Mealy




“Moore Machine”  
developed in 1956  
by Edward F. Moore

# Mealy vs Moore

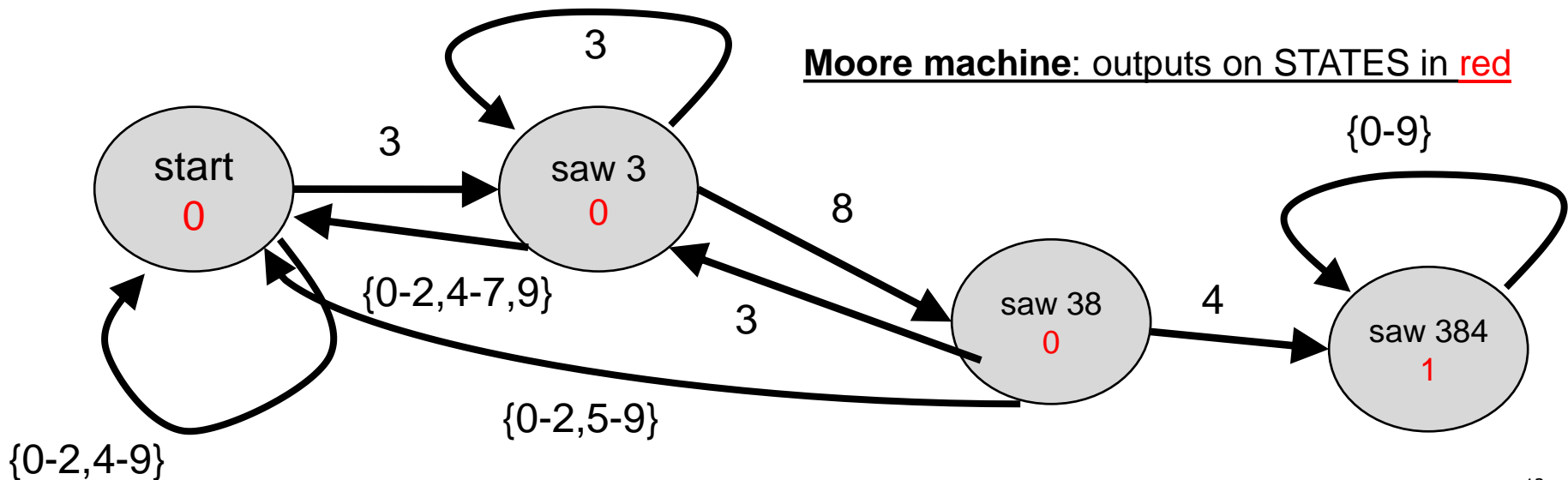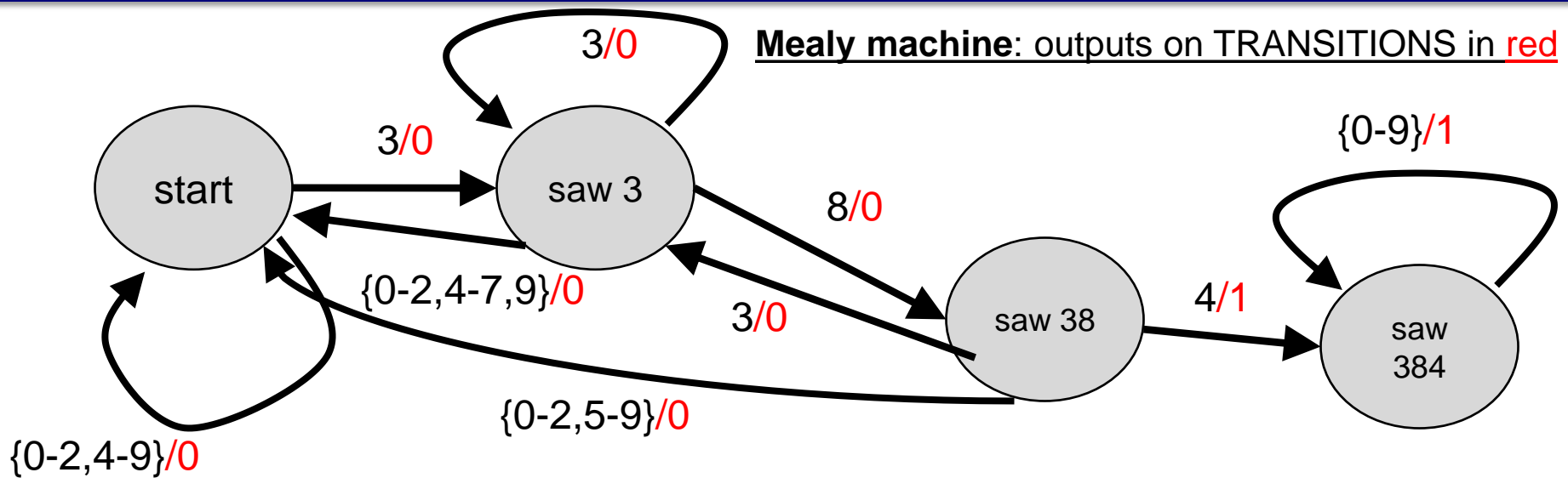


# State Transition Diagram → Truth Table

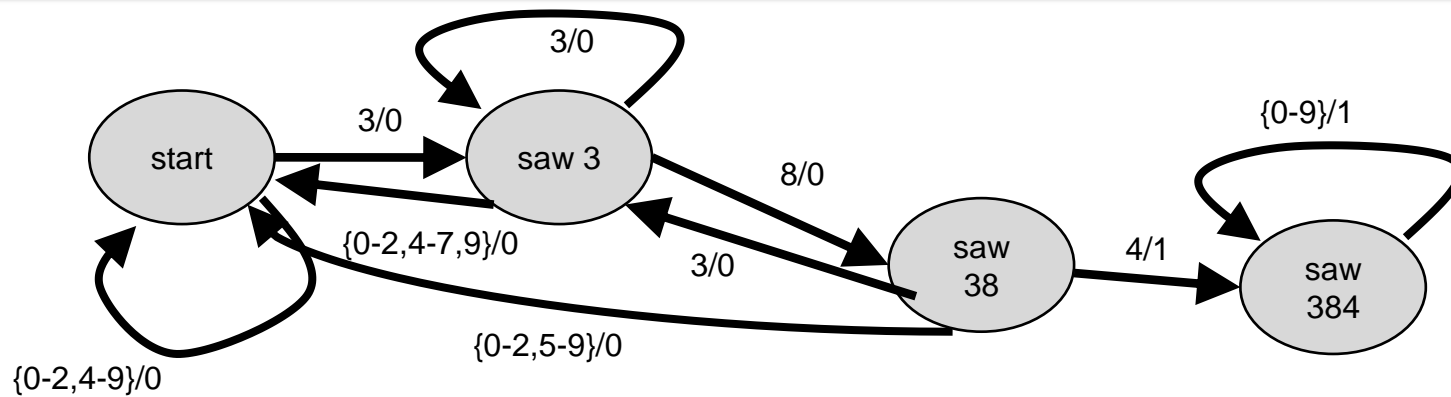

Current State	Input	Next state	Output
Start	3	Saw 3	0 (closed)
Start	Not 3	Start	0
Saw 3	8	Saw 38	0
Saw 3	3	Saw 3	0
Saw 3	Not 8 or 3	Start	0
Saw 38	4	Saw 384	1 (open)
Saw 38	3	Saw 3	0
Saw 38	Not 4 or 3	Start	0
Saw 384	Any	Saw 384	1

# State Transition Diagram → Truth Table

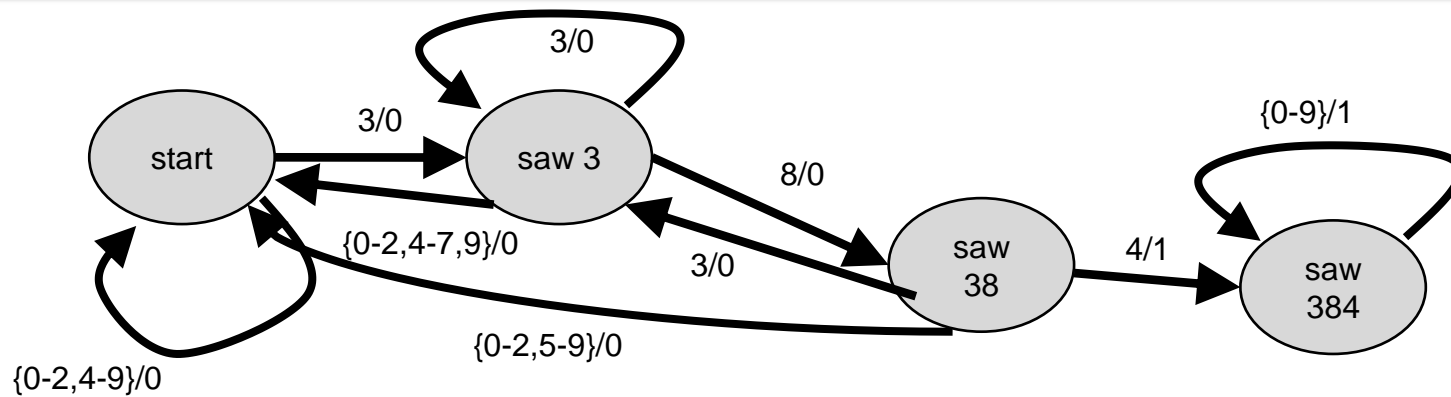

Digital logic → must represent everything in binary, including state names.  
But mapping is arbitrary!

We'll use this mapping:

start = 00

saw 3 = 01

saw 38 = 10

saw 384 = 11

# State Transition Diagram → Truth Table

Current State	Input	Next state	Output
00 (start)	3	01	0 (closed)
00	Not 3	00	0
01	8	10	0
01	3	01	0
01	Not 8 or 3	00	0
10	4	11	1 (open)
10	3	01	0
10	Not 4 or 3	00	0
11	Any	11	1

4 states → 2 flip-flops to hold the current state of the FSM

inputs to flip-flops are  $D_1D_0$

outputs of flip-flops are  $Q_1Q_0$

# State Transition Diagram → Truth Table

Q1	Q0	Input	D1	D0	Output
0	0	3	0	1	0 (closed)
0	0	Not 3	0	0	0
0	1	8	1	0	0
0	1	3	0	1	0
0	1	Not 8 or 3	0	0	0
1	0	4	1	1	1 (open)
1	0	3	0	1	0
1	0	Not 4 or 3	0	0	0
1	1	Any	1	1	1

Input can be 0-9 → requires 4 bits  
input bits are in3, in2, in1, in0



# State Transition Diagram → Truth Table

Q1	Q0	In3	In2	In1	In0	D1	D0	Output
0	0	0	0	1	1	0	1	0
0	0	Not 3 (all binary combos other than 0011)				0	0	0
0	1	1	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
0	1	Not 8 or 3 (all binary combos other than 1000 & 0011)				0	0	0
1	0	0	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	Not 4 or 3 (all binary combos other than 0100 & 0011)				0	0	0
1	1	Any				1	1	1

From here, it's just like combinational logic design!  
Write out product-of-sums equations, optimize, and build.

# State Transition Diagram → Truth Table

Q1	Q0	In3	In2	In1	In0	D1	D0	Output
0	0	0	0	1	1	0	1	0
0	0	Not 3				0	0	0
0	1	1	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
0	1	Not 8 or 3				0	0	0
1	0	0	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	Not 4 or 3				0	0	0
1	1	Any				1	1	1

Output =  $(Q1 \ \& \ !Q0 \ \& \ !In3 \ \& \ In2 \ \& \ !In1 \ \& \ !In0) \ | \ (Q1 \ \& \ Q0)$

D1 =  $(!Q1 \ \& \ Q0 \ \& \ In3 \ \& \ !In2 \ \& \ !In1 \ \& \ !In0) \ | \ (Q1 \ \& \ !Q0 \ \& \ !In3 \ \& \ In2 \ \& \ !In1 \ \& \ !In0) \ | \ (Q1 \ \& \ Q0)$

D0 = do the same thing

# State Transition Diagram → Truth Table


Q1	Q0	In3	In2	In1	In0	D1	D0	Output
0	0	0	0	1	1	0	1	0
0	0	Not 3				0	0	0
0	1	1	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
0	1	Not 8 or 3				0	0	0
1	0	0	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0
1	0	Not 4 or 3				0	0	0
1	1	Any				1	1	1

Remember, these represent **DFF outputs**

...and these are the **DFF inputs**


The DFFs are how we store the **state**.

# Truth Table → Sequential Circuit

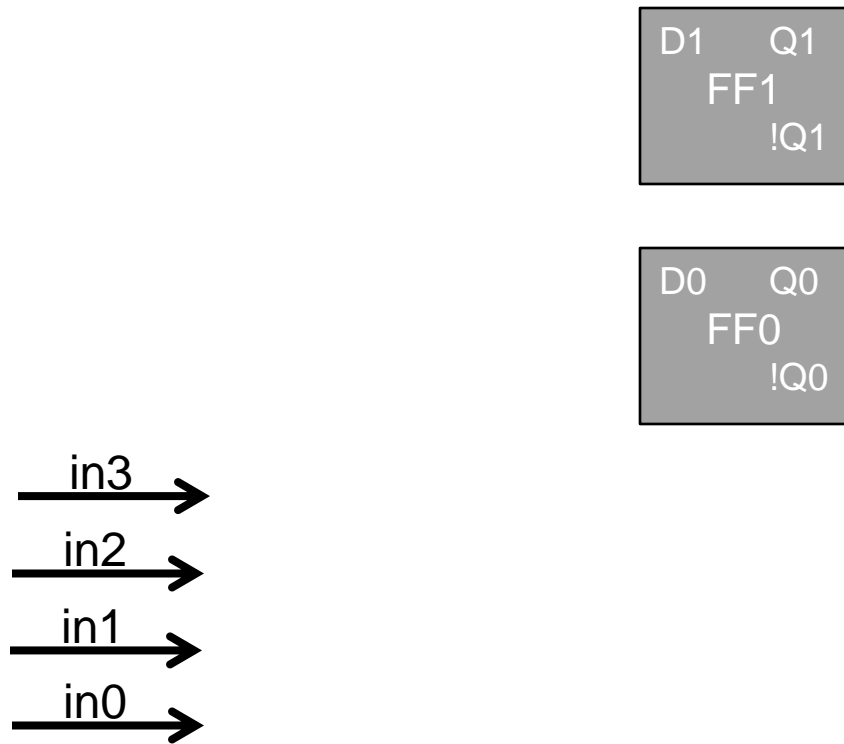


Start with 2 FFs and 4 input bits. FFs hold current state of FSM.  
(not showing clock/enable inputs on flip flops)

# Truth Table → Sequential Circuit

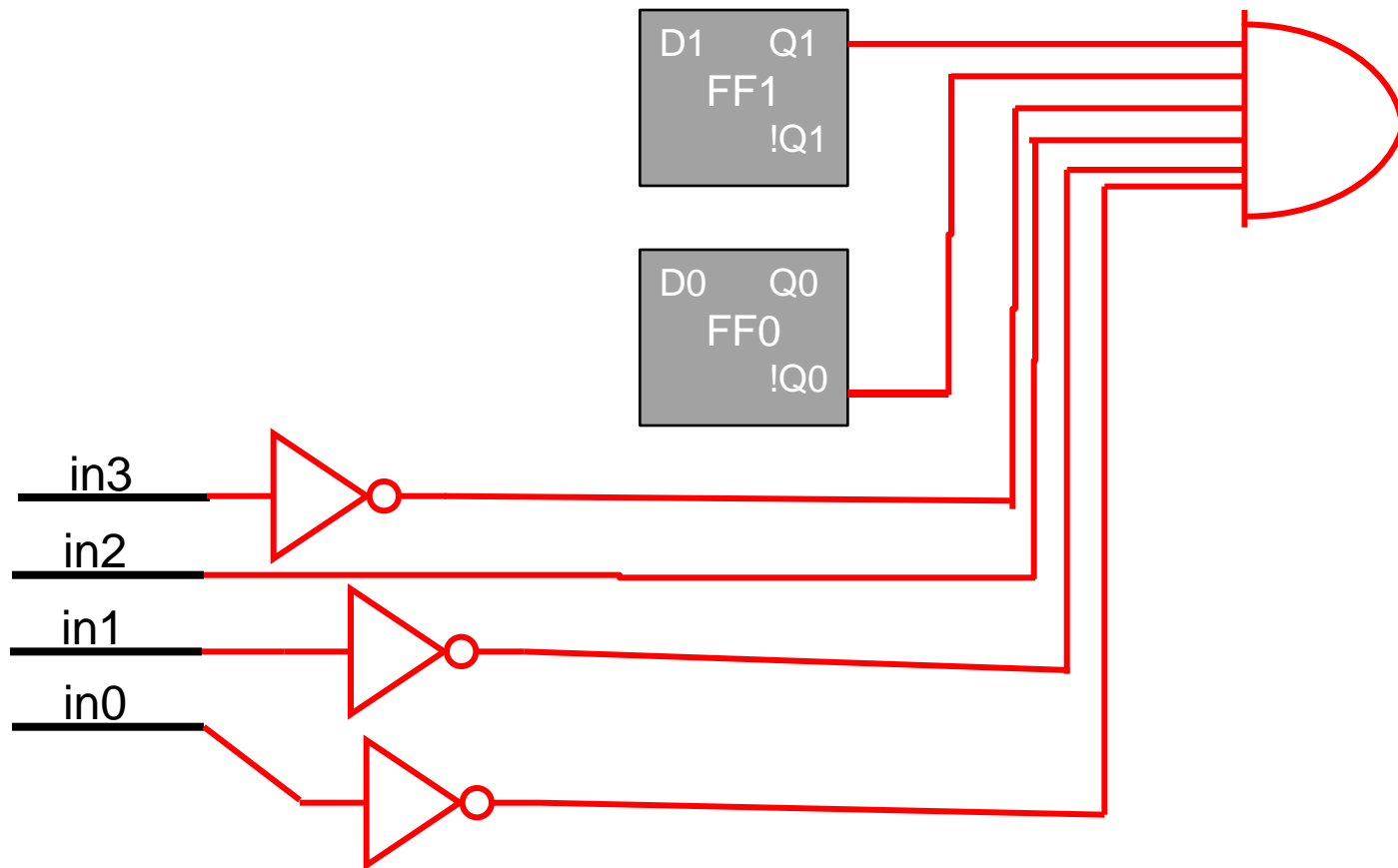


$$\text{output} = (Q1 \ \& \ !Q0 \ \& \ !\text{in3} \ \& \ \text{in2} \ \& \ !\text{in1} \ \& \ !\text{in0}) \mid (Q1 \ \& \ Q0)$$

# Truth Table → Sequential Circuit

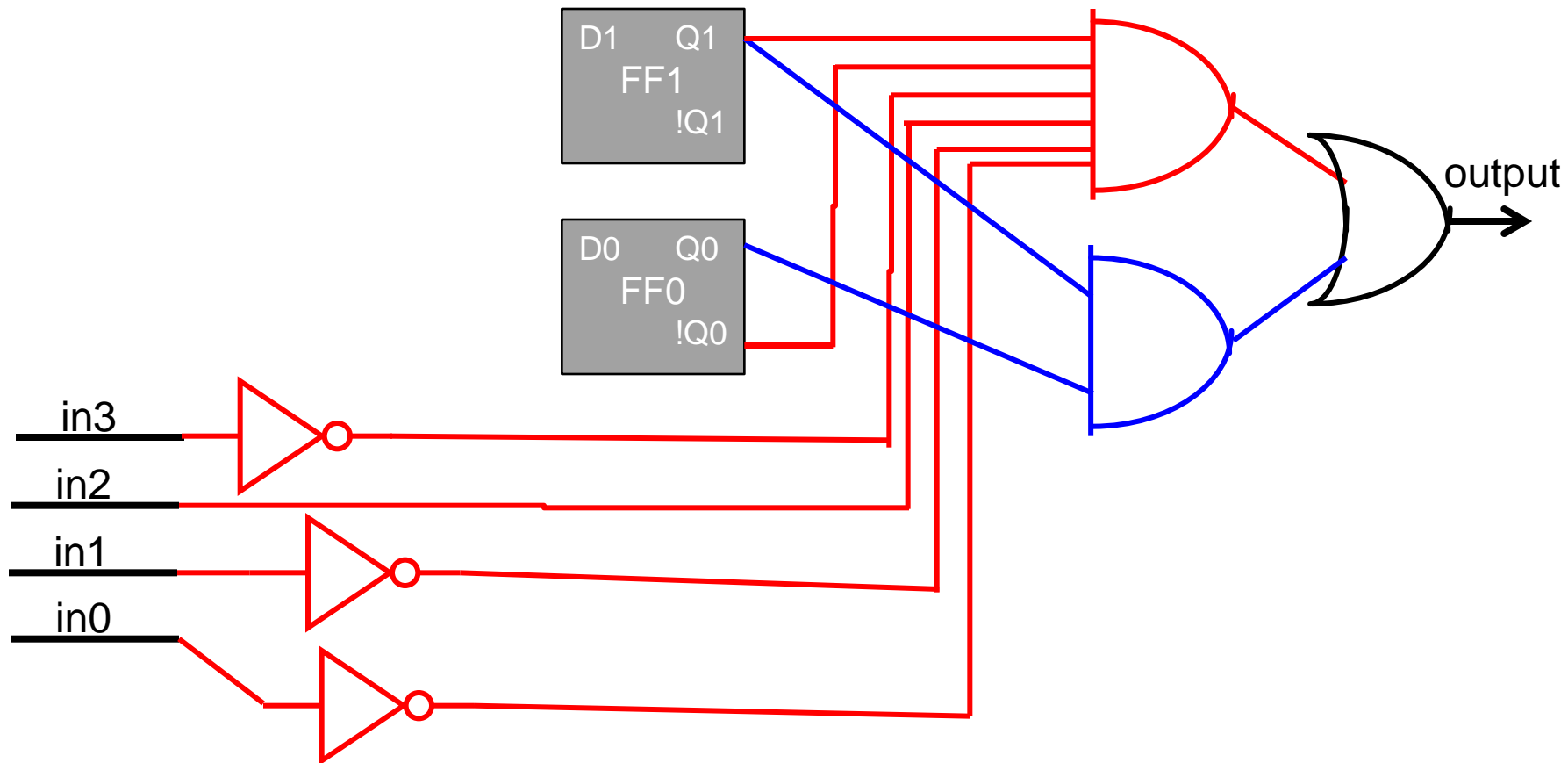

$$\text{output} = (Q1 \ \& \ !Q0 \ \& \ !in3 \ \& \ in2 \ \& \ !in1 \ \& \ !in0) \mid (Q1 \ \& \ Q0)$$

# Truth Table → Sequential Circuit

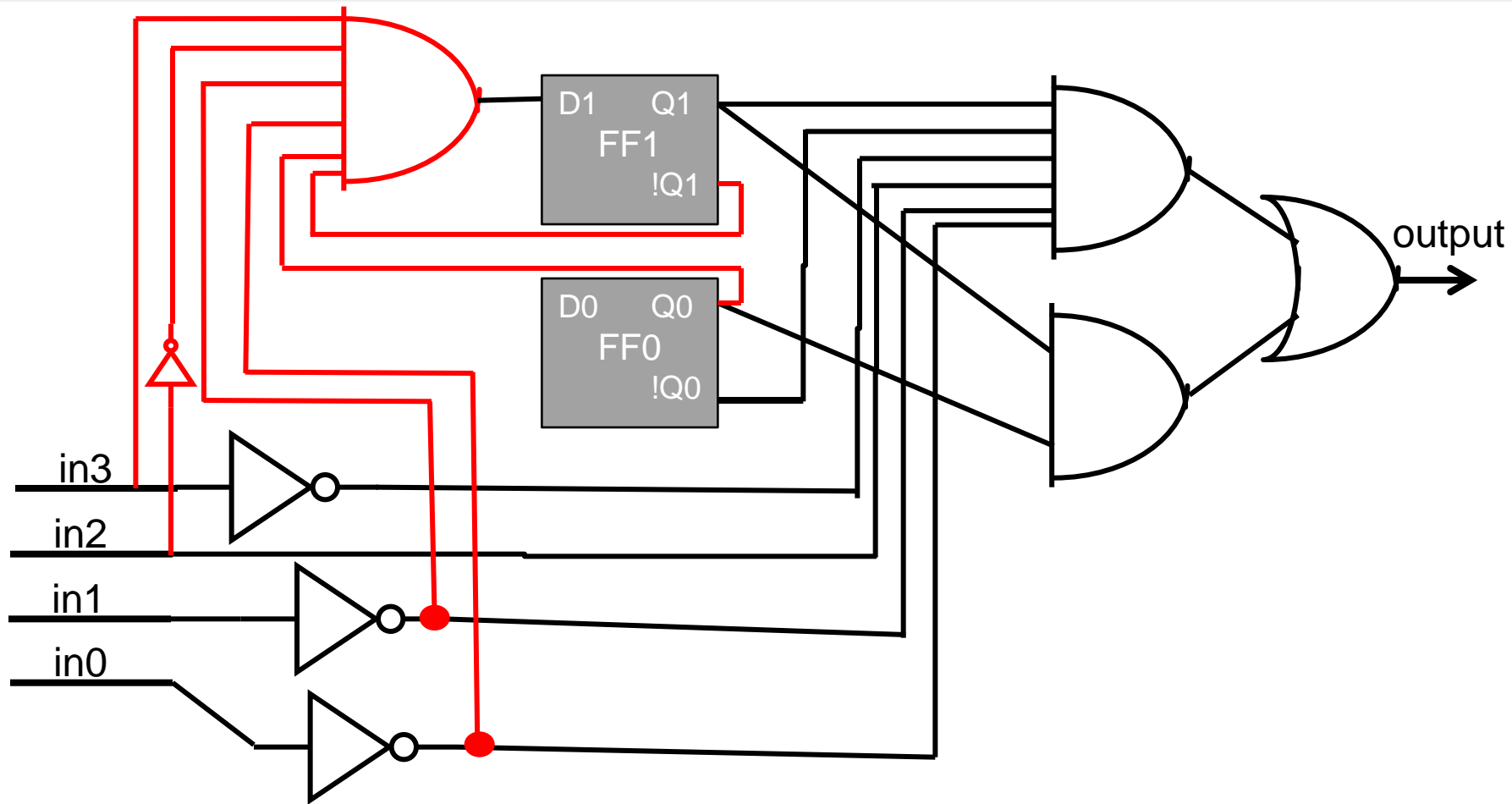

$$D1 = (!Q1 \& Q0 \& \text{in3} \& !\text{in2} \& !\text{in1} \& !\text{in0}) \mid (Q1 \& !Q0 \& !\text{in3} \& \text{in2} \& !\text{in1} \& !\text{in0}) \mid (Q1 \& Q0)$$

*Not pictured*

Follow a similar procedure for D0...

# FSM Design Principles

- Systematic approach that always works:
  - Start with state transition diagram
  - Make truth table
  - Write out sum-of-products logic equations
  - Optimize logic equations (optional)
  - Implement logic in circuit
- Sometimes can do something non-systematic
  - Requires cleverness, but tough to do in general
- Do not do any of the following!
  - Use clock as an input (D input of FF)
  - Perform logic on clock signal  
(except maybe a NOT gate to go from rising to falling edge triggered)