

ECE/CS 250

Computer Architecture

Fall 2021

Processor Design: Datapath and Control


Tyler Bletsch
Duke University

Slides are derived from work by
Daniel J. Sorin (Duke), Amir Roth (Penn)

Where We Are in This Course Right Now

- So far:
 - We know what a computer architecture is
 - We know what kinds of instructions it might execute
 - We know how to perform arithmetic and logic in an ALU
- Now:
 - We learn how to design a processor in which the ALU is just one component
 - Processor must be able to fetch instructions, decode them, and execute them
 - There are many ways to do this, even for a given ISA
- Next:
 - We learn how to design memory systems

This Unit: Processor Design

 

- Datapath components and timing
 - Registers and register files
 - Memories (RAMs)
- Mapping an ISA to a datapath
- Control
- Exceptions


Readings

- Patterson and Hennessy
 - Chapter 4: Sections 4.1-4.4
- Read this chapter carefully
 - It has many more examples than I can cover in class

So You Have an ALU...

- **Important reminder:** a processor is just a big finite state machine (FSM) that interprets some ISA
- Start with one instruction
 - `add $3, $2, $4`
 - ALU performs just a small part of execution of instruction
 - You have to read and write registers
 - You have have to fetch the instruction to begin with
- What about loads and stores?
 - Need some sort of memory interface
- What about branches?
 - Need some hardware for that, too

Datapath and Control

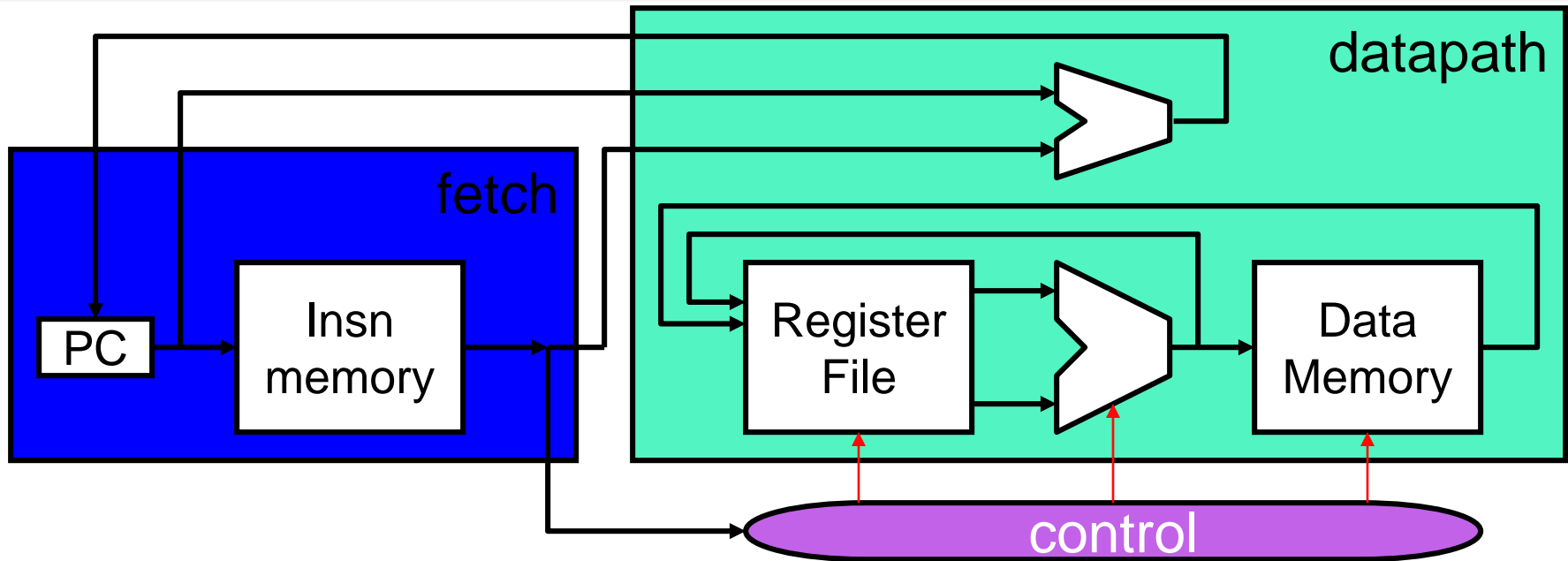

- **Datapath**: registers, memories, ALUs (computation)
- **Control**: which registers read/write, which ALU operation
- **Fetch**: get instruction, translate into control
- Processor Cycle: **Fetch** → **Decode** → **Execute**

Building a Processor for an ISA

- Fetch is pretty straightforward
 - Just need a register (called the Program Counter or PC) to hold the next address to fetch from instruction memory
 - Provide address to instruction memory → instruction memory provides instruction at that address
- Let's start with the datapath
 1. Look at ISA
 2. Make sure datapath can implement every instruction

Datapath for MIPS ISA

- Consider only the following instructions

```
add $1,$2,$3
```

```
addi $1,$2,<value>
```

```
lw $1,4($3)
```


```
sw $1,4($3)
```

```
beq $1,$2,PC_relative_target
```

```
j Absolute_target
```

- Why only these?
 - Most other instructions are similar from datapath viewpoint
 - I leave the ones that aren't for you to figure out


Review: A Register

 

Note: Above is the "classic" register we learned before; we're just introducing a new symbol for the same thing


- **Register:** DFF array with shared clock, write-enable (WE)
 - Notice: both a clock and a WE ($DFF_{WE} = \text{clock} \ \& \ \text{register}_{WE}$)
 - Convention I: clock represented by wedge
 - Convention II: if no WE, DFF is written on every clock

Uses of Registers

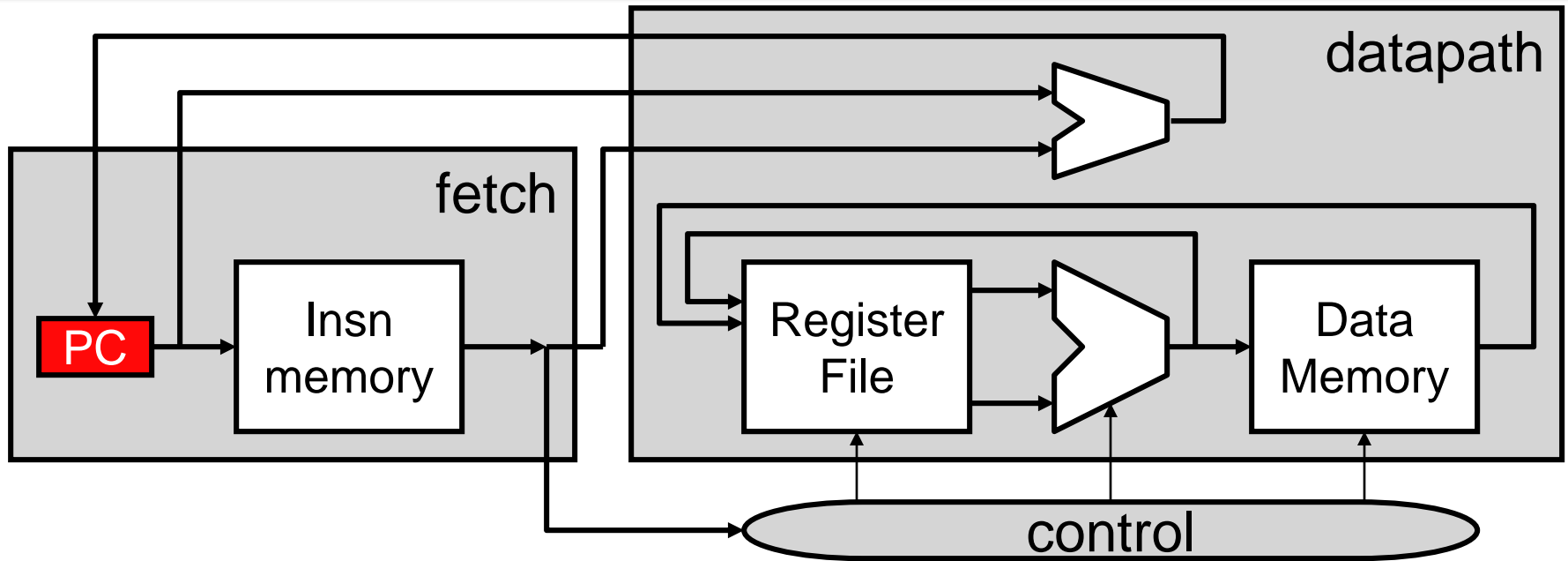

- A single register is good for some things
 - PC: program counter
 - Other things which aren't the ISA registers (more later in semester)


What About the ISA Registers?

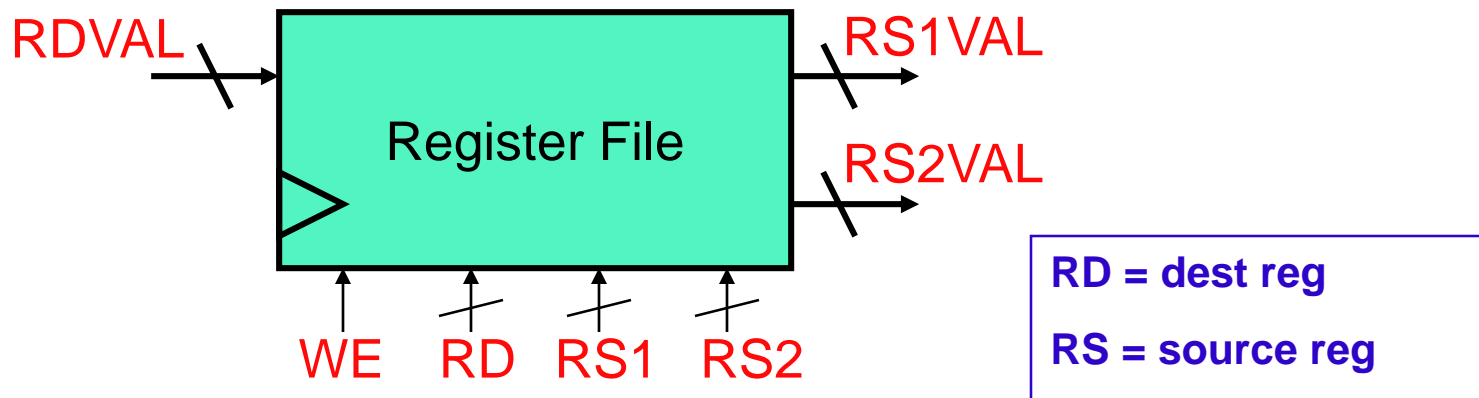


- **Register file**: the ISA (“architectural”, “visible”) registers
 - Two read “ports” + one write “port”
 - Maximum number of reads/writes in single instruction (R-type)
- **Port**: wires for accessing an array of data
 - Data bus: width of data element (MIPS: 32 bits)
 - Address bus: width of \log_2 number of elements (MIPS: 5 bits)
 - Write enable: if it’s a write port
 - M ports = M parallel and independent accesses

Reminder

Register File With Tri-State Read Ports

 

Another Useful Component: Memory

 


- **Memory**: where instructions and data reside
 - One read/write "port": one access per cycle, either read **or** write
 - One address bus
 - One input data bus for writes, one output data bus for reads
- Actually, a more traditional definition of memory is
 - One input/output data bus
 - No clock → asynchronous "strobe" instead

Dramatis Personae


Register




Memory

 

Register File

 

Arithmetic Logic Unit

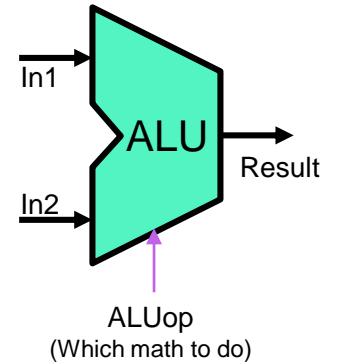

Shift left by two bits



Adder



Adder that always adds 4




Sign extender



Converts to longer bit widths; preserves sign
 (3) 0011 => 00000011 (still 3)
 (-5) 1011 => 11111011 (still -5)

Mux

 


Plain ol' AND gate




Let's Build A MIPS-like Datapath

Start With Fetch

 


- PC and instruction memory
- A +4 incrementer computes default next instruction PC
 - Why +4 (and not +1)? What will it be for 16-bit Duke 250/16?

First Instruction: add \$rd, \$rs, \$rt

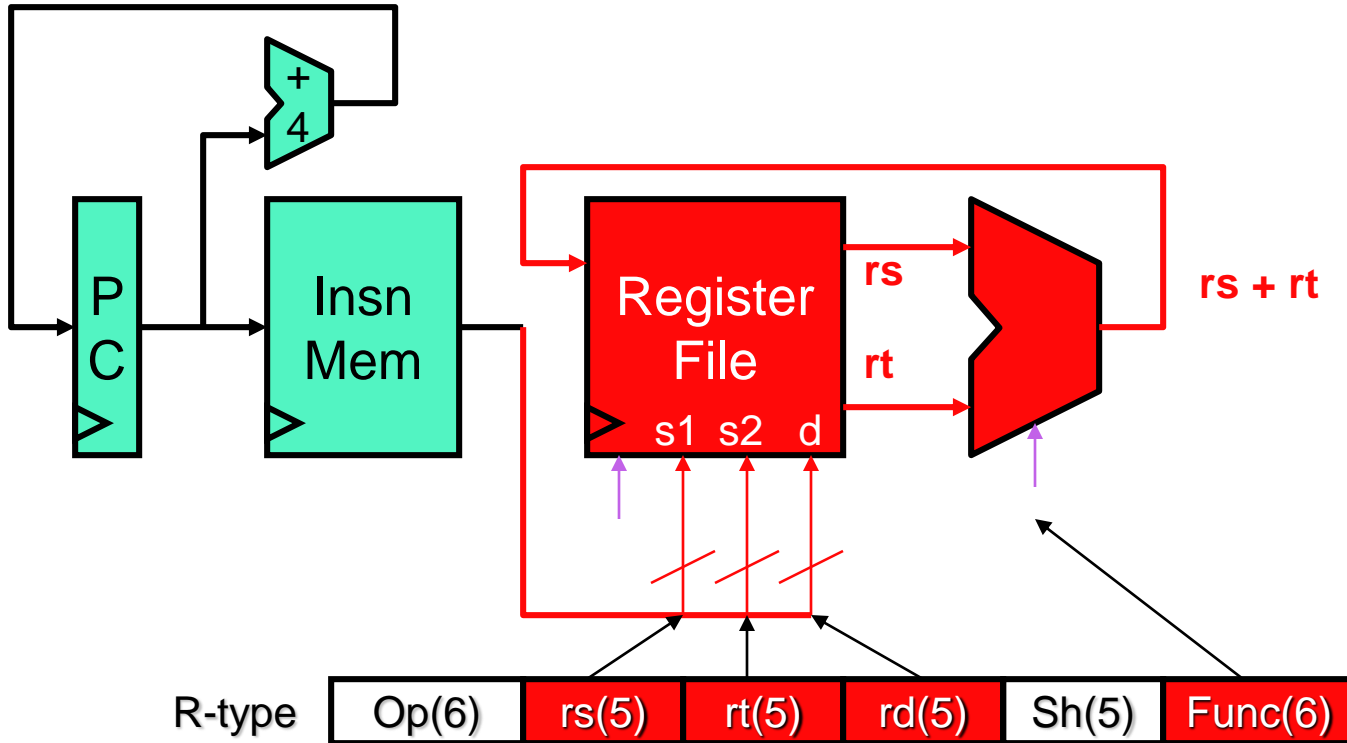


- Add register file and ALU

Second Instruction: addi \$rt, \$rs, imm

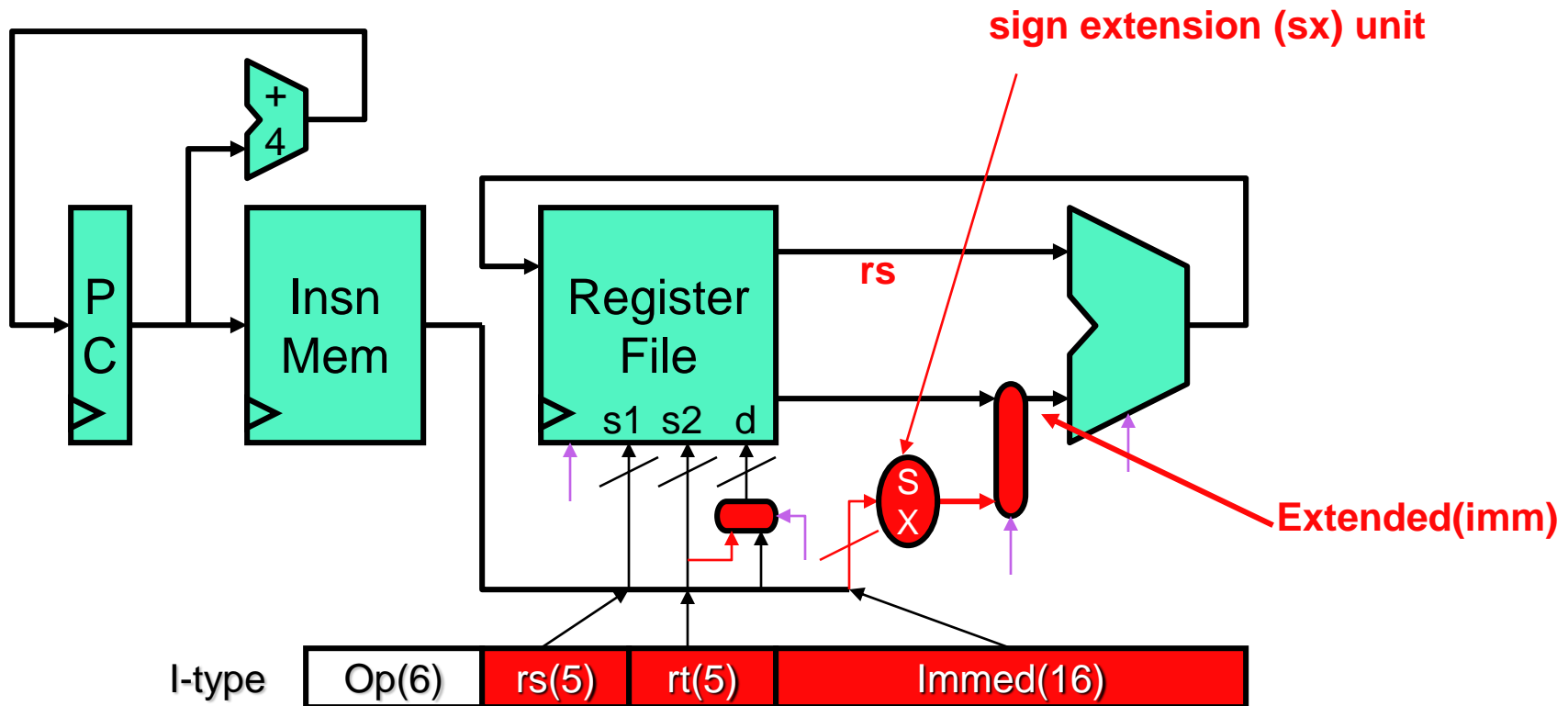


- Destination register can now be either rd or rt
- Add sign extension unit and mux into second ALU input

Third Instruction: lw \$rt, imm(\$rs)

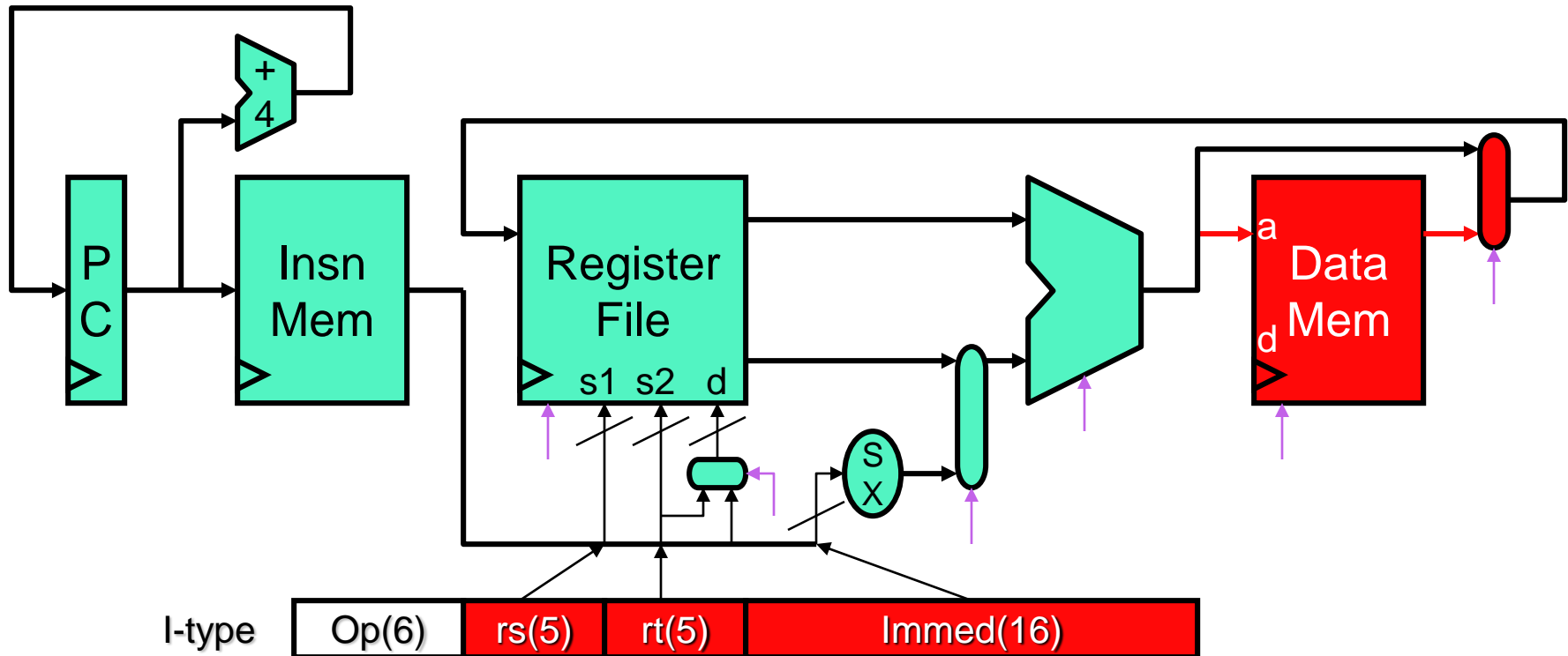


- Add data memory, address is ALU output ($rs+imm$)
- Add register write data mux to select memory output or ALU output

Fourth Instruction: sw \$rt, imm(\$rs)

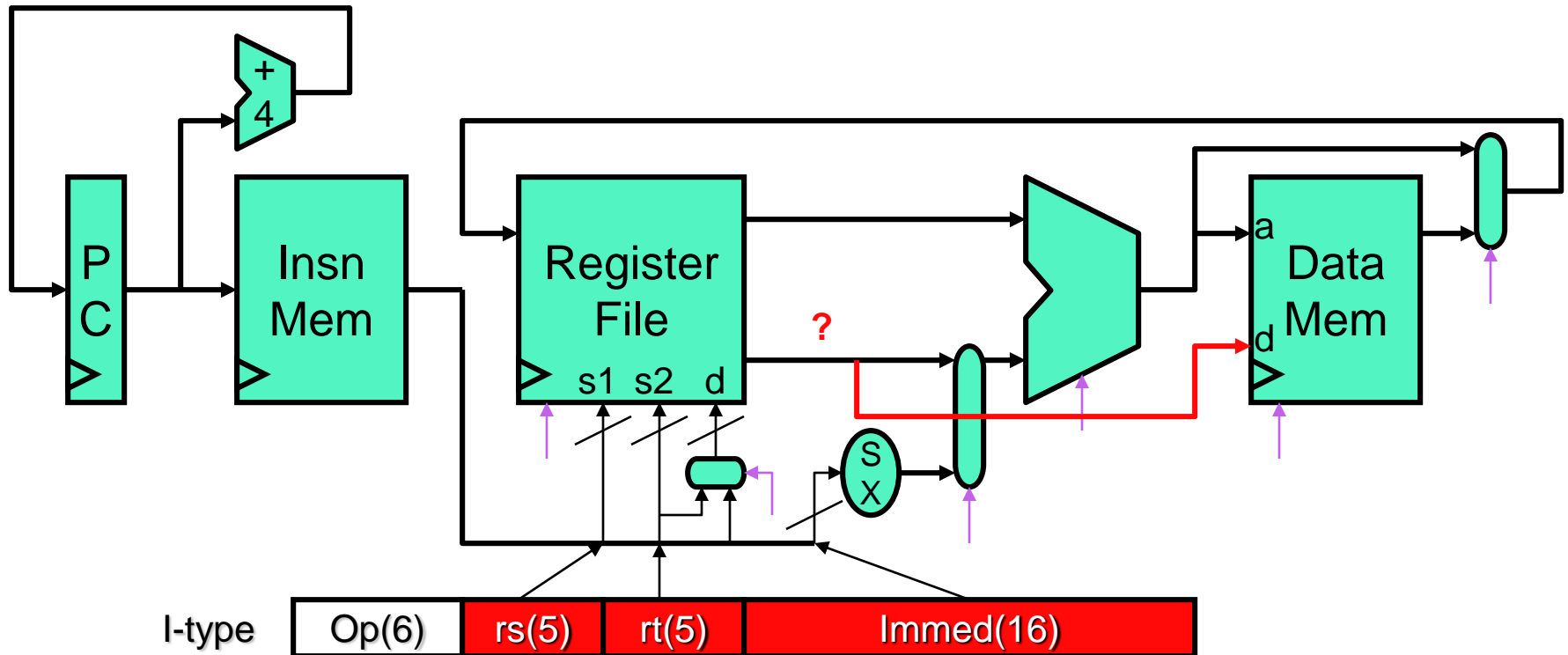


- Add path from second input register to data memory data input
- Disable RegFile's WE signal

Fifth Instruction: beq \$1, \$2, target

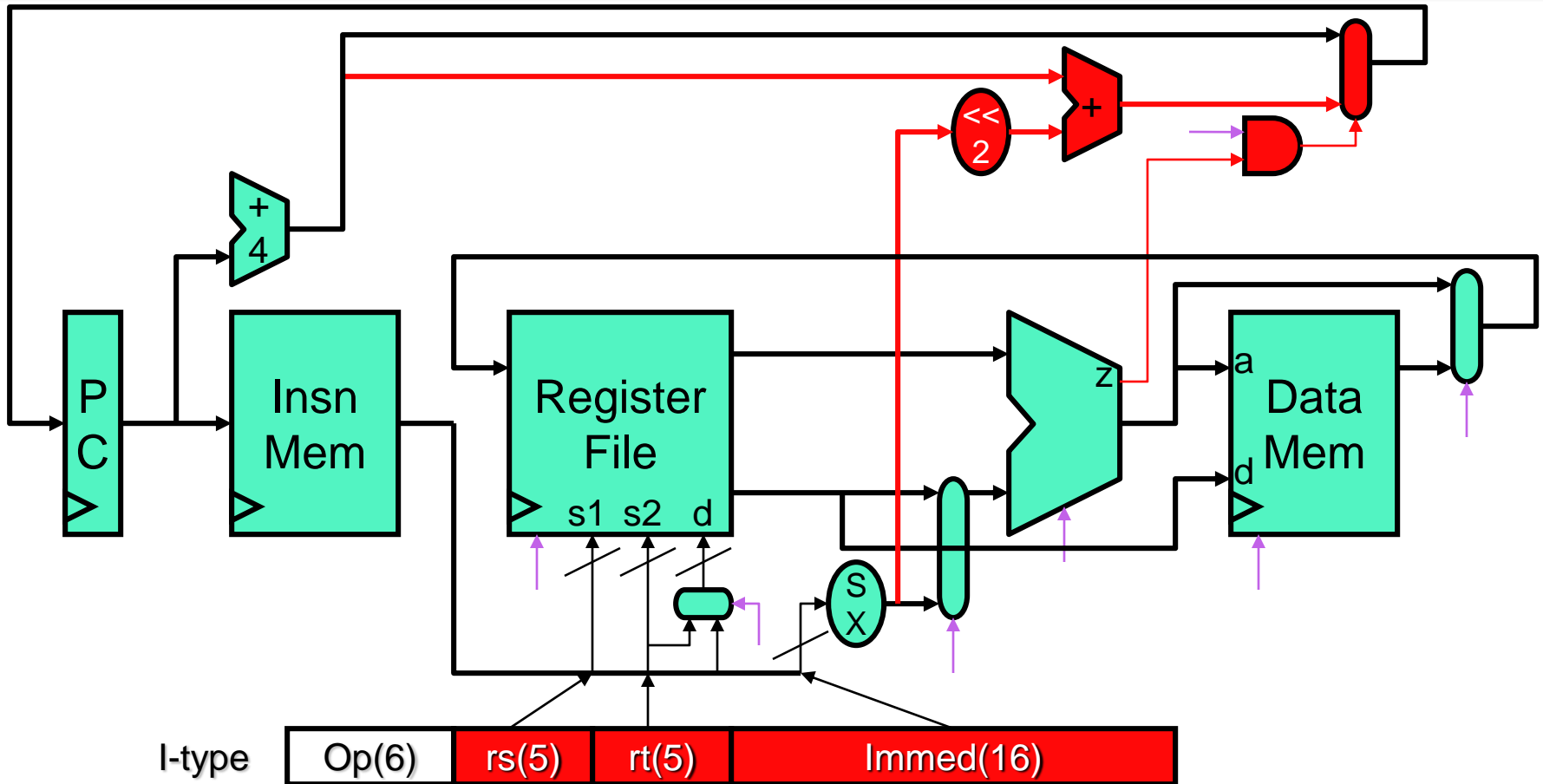

- Add left shift unit (why?) and adder to compute PC-relative branch target
- Add mux to do what?

Sixth Instruction: j

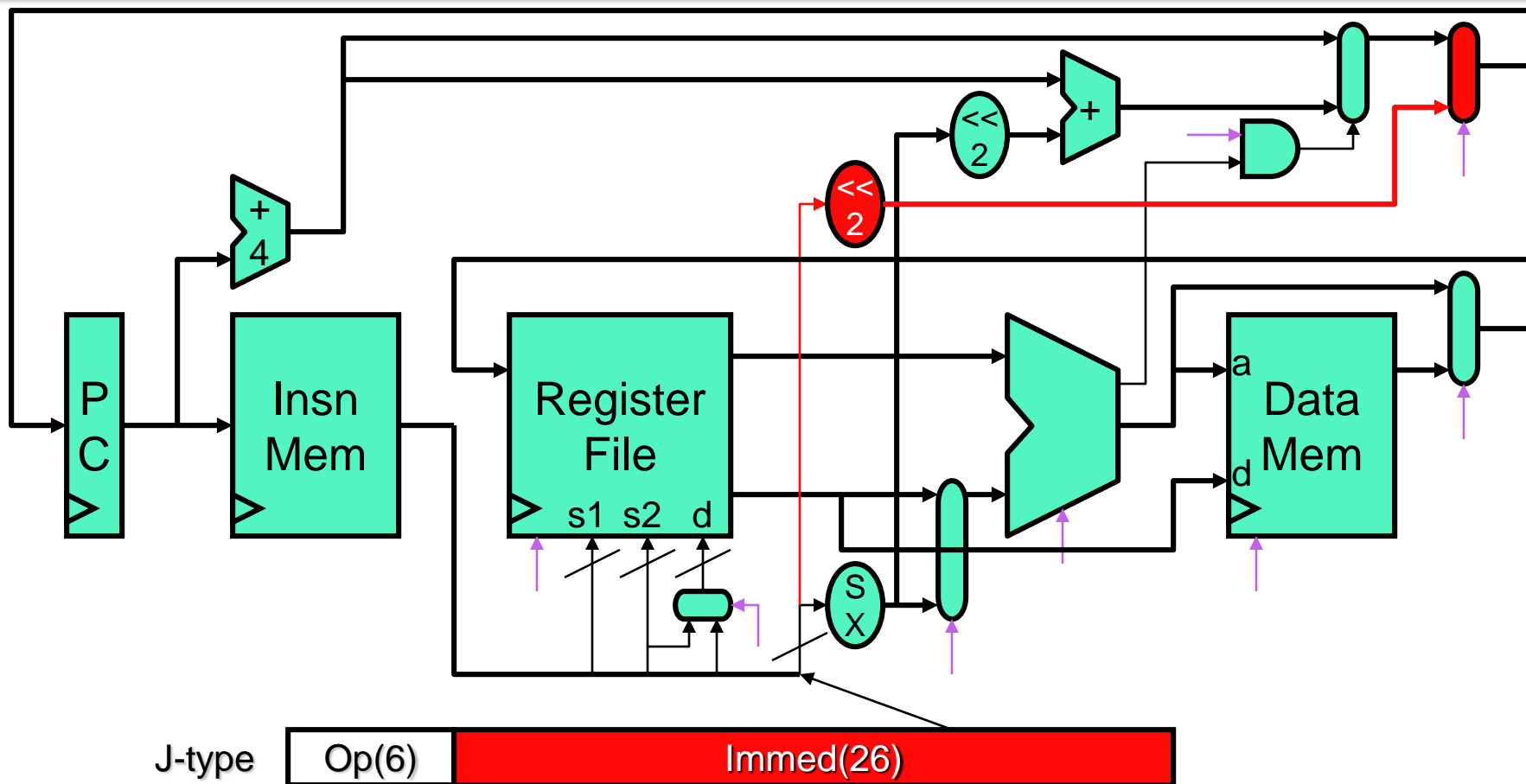

- Add shifter to compute left shift of 26-bit immediate
- Add additional PC input mux for jump target

Seventh, Eight, Ninth Instructions

- Are these the paths we would need for all instructions?

sll \$1,\$2,4 // shift left logical

- Like an arithmetic operation, but need a shifter too

slt \$1,\$2,\$3 // set less than (slt)

- Like subtract, but need to write the condition bits, not the result
 - Need zero extension unit for condition bits
 - Need additional input to register write data mux

jal absolute_target // jump and link

- Like a jump, but also need to write PC+4 into \$ra (\$31)
 - Need path from PC+4 adder to register write data mux
 - Need to be able to specify \$31 as an implicit destination


jr \$31 // jump register

- Like a jump, but need path from register read to PC write mux

Clock Timing


- Must deliver clock(s) to avoid races
- Can't write and read same value at same clock edge
 - Particularly a problem for RegFile and Memory
- May create multiple clock edges (from single input clock) by using buffers (to delay clock) and inverters
- For Homework 4 (the Duke 250/16 CPU):
 - Keep the clock SIMPLE and GLOBAL
 - You may need to do the PC on *falling* edge and everything else on *rising* edge
 - Changing clock edges in this way will separate PC++ from logic
 - Otherwise, if the PC changes *while* the operation is occurring, the instruction bits will change before the answer is computed -> *non-deterministic behavior* ☹️
 - Note: A cheap way to make something trigger on the other clock edge is to NOT the clock on the way in to that component

This Unit: Processor Design

 


- Datapath components and timing
 - Registers and register files
 - Memories (RAMs)
 - Clocking strategies
- Mapping an ISA to a datapath
- Control
- Exceptions

↑ What Is Control? ↑

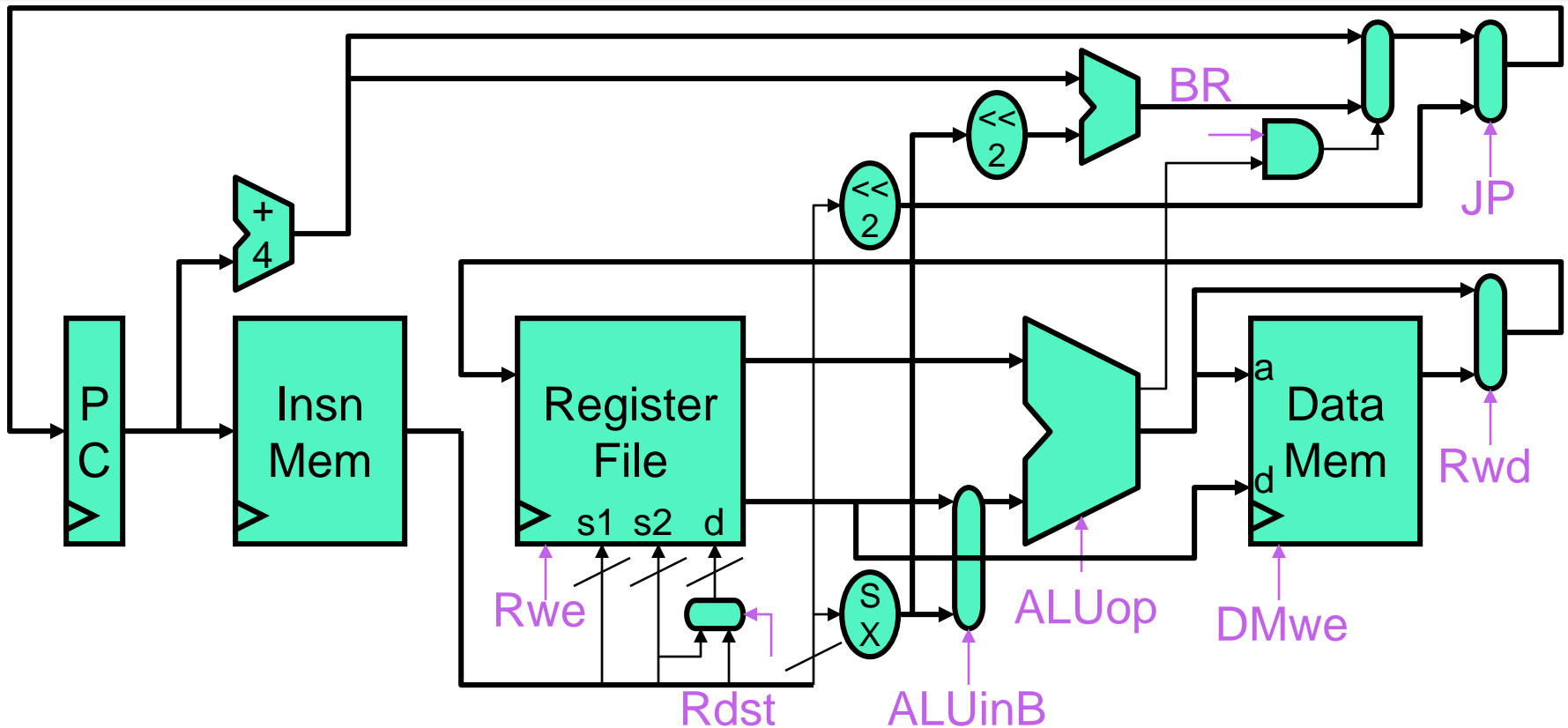


- 9 signals control flow of data through this datapath
 - MUX selectors, or register/memory write enable signals
 - Datapath of current microprocessor has 100s of control signals

Example: Control for add

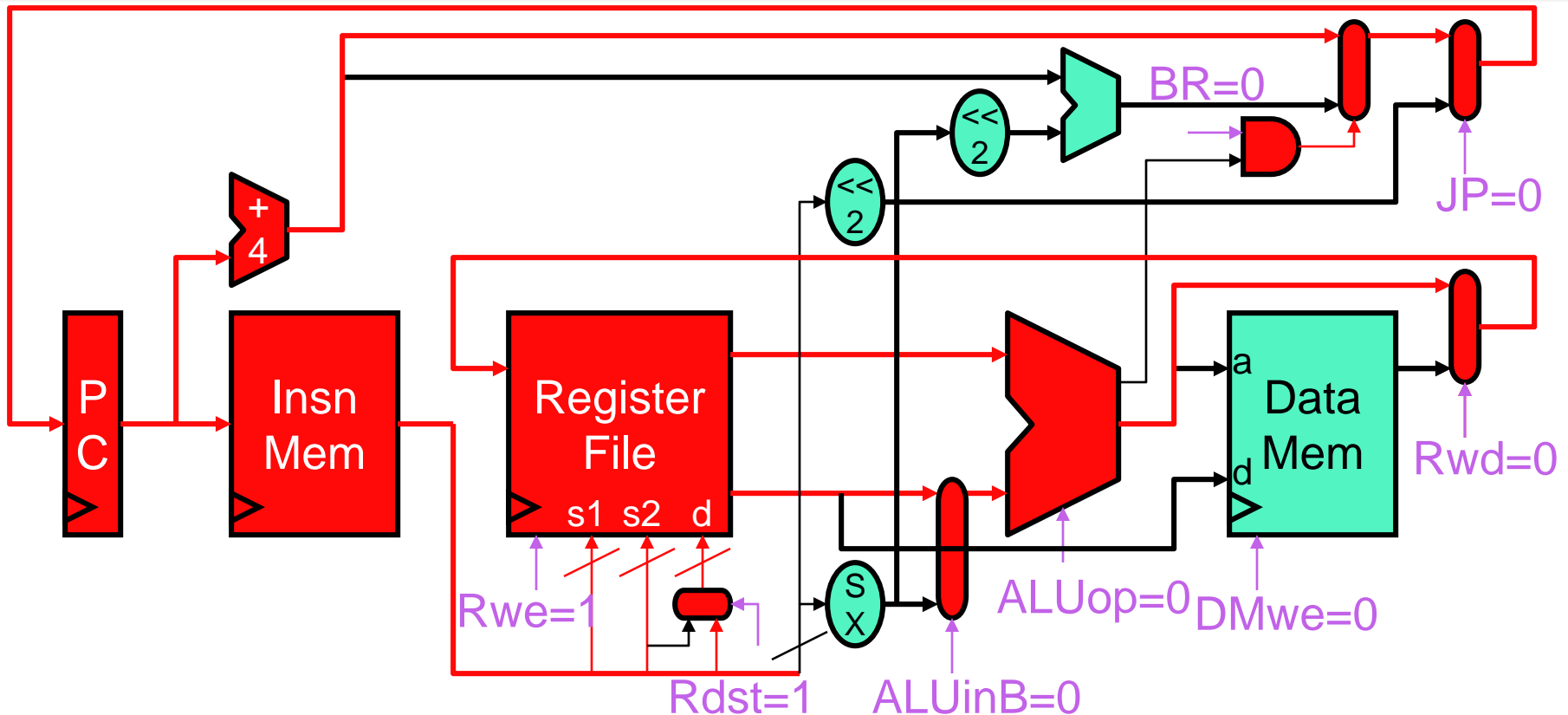


- **Rwe:** Register Write Enable
- **Rdst:** Register Destination chooser
- **ALUinB:** ALU input B chooser
- **ALUOp:** ALU operation (multi-bit)
- **DMwe:** Data Memory Write Enable
- **Rwd:** Register Write Data chooser
- **BR:** Branch?
- **JP:** Jump?

Example: Control for sw

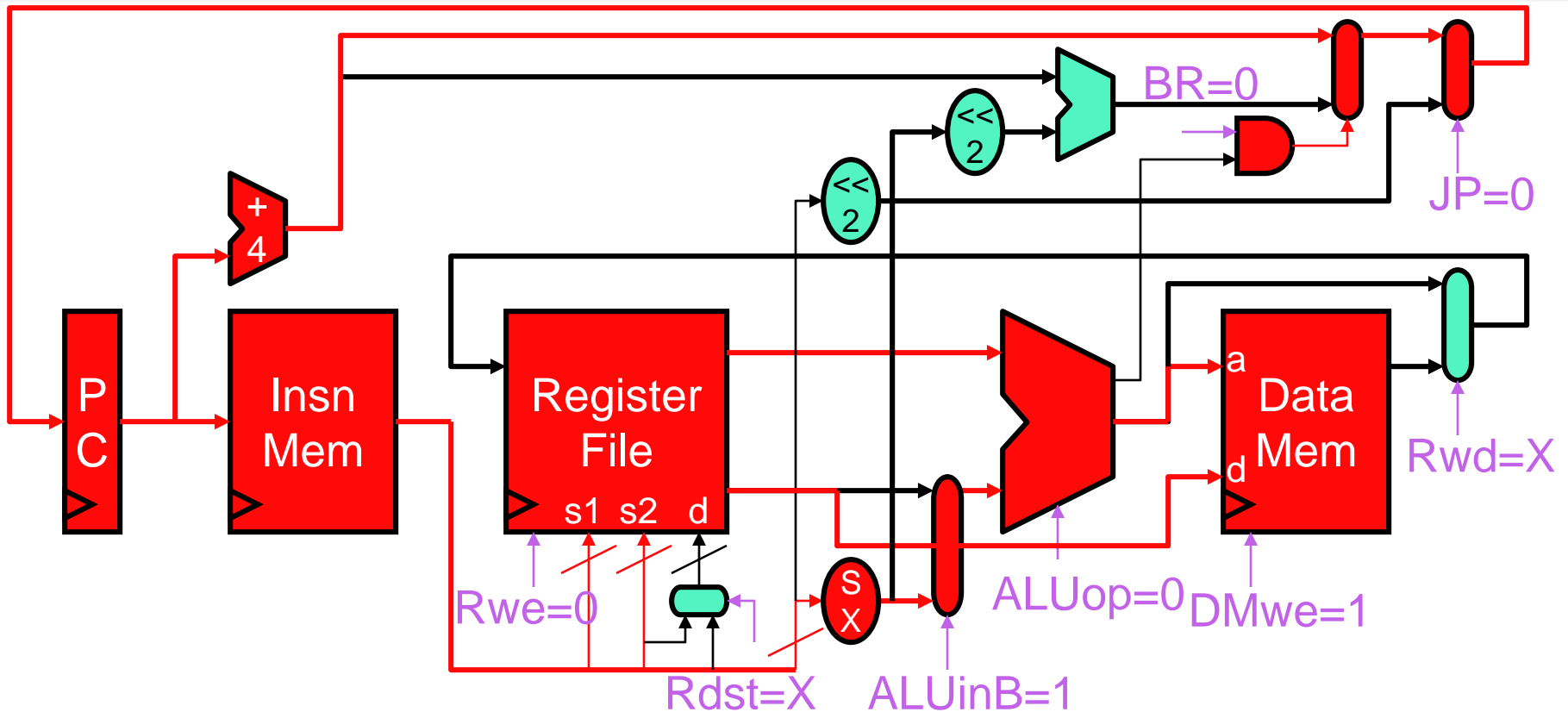


- Difference between a sw and an add is 5 signals
 - 3 if you don't count the X ("don't care") signals

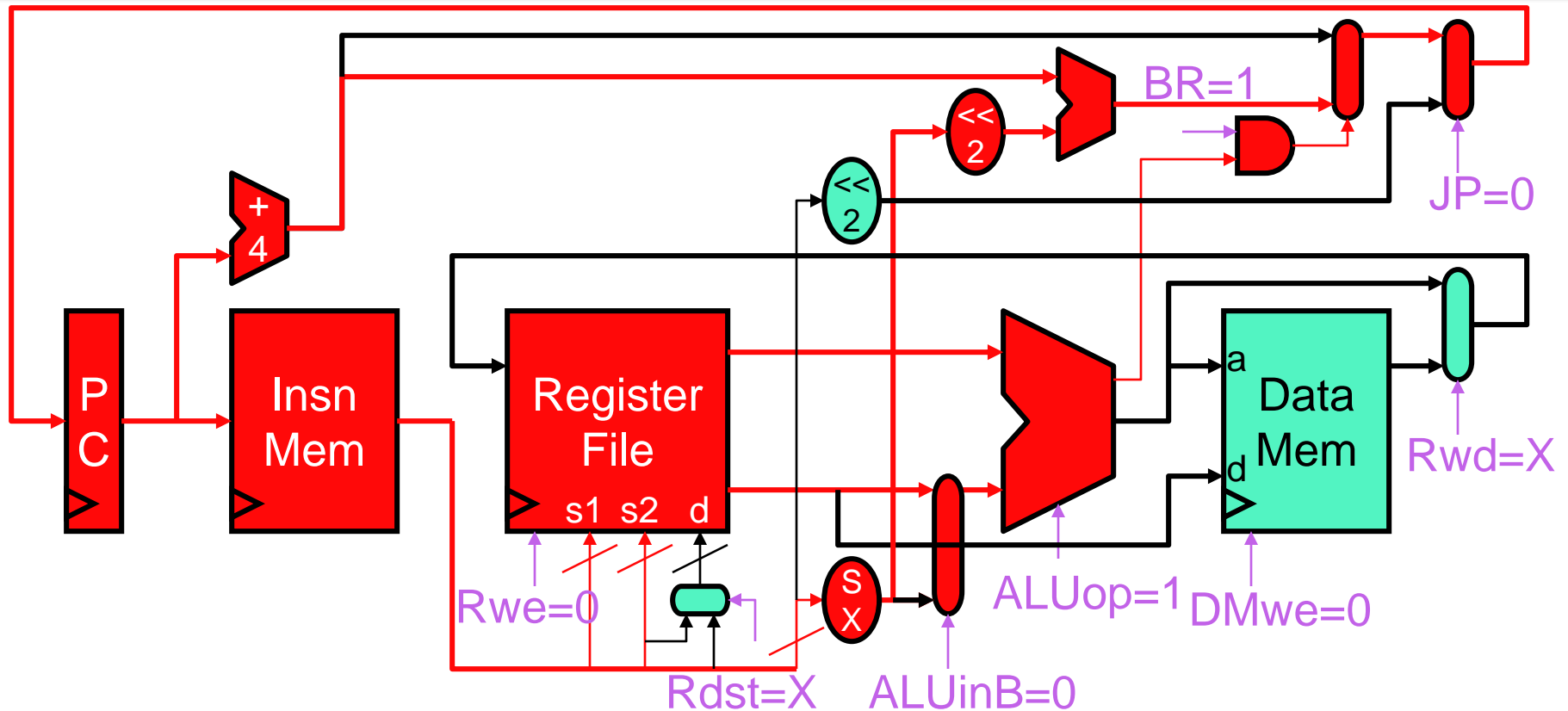Example: Control for beq \$1, \$2, target



- Difference between a store and a branch is only 4 signals

How Is Control Implemented?

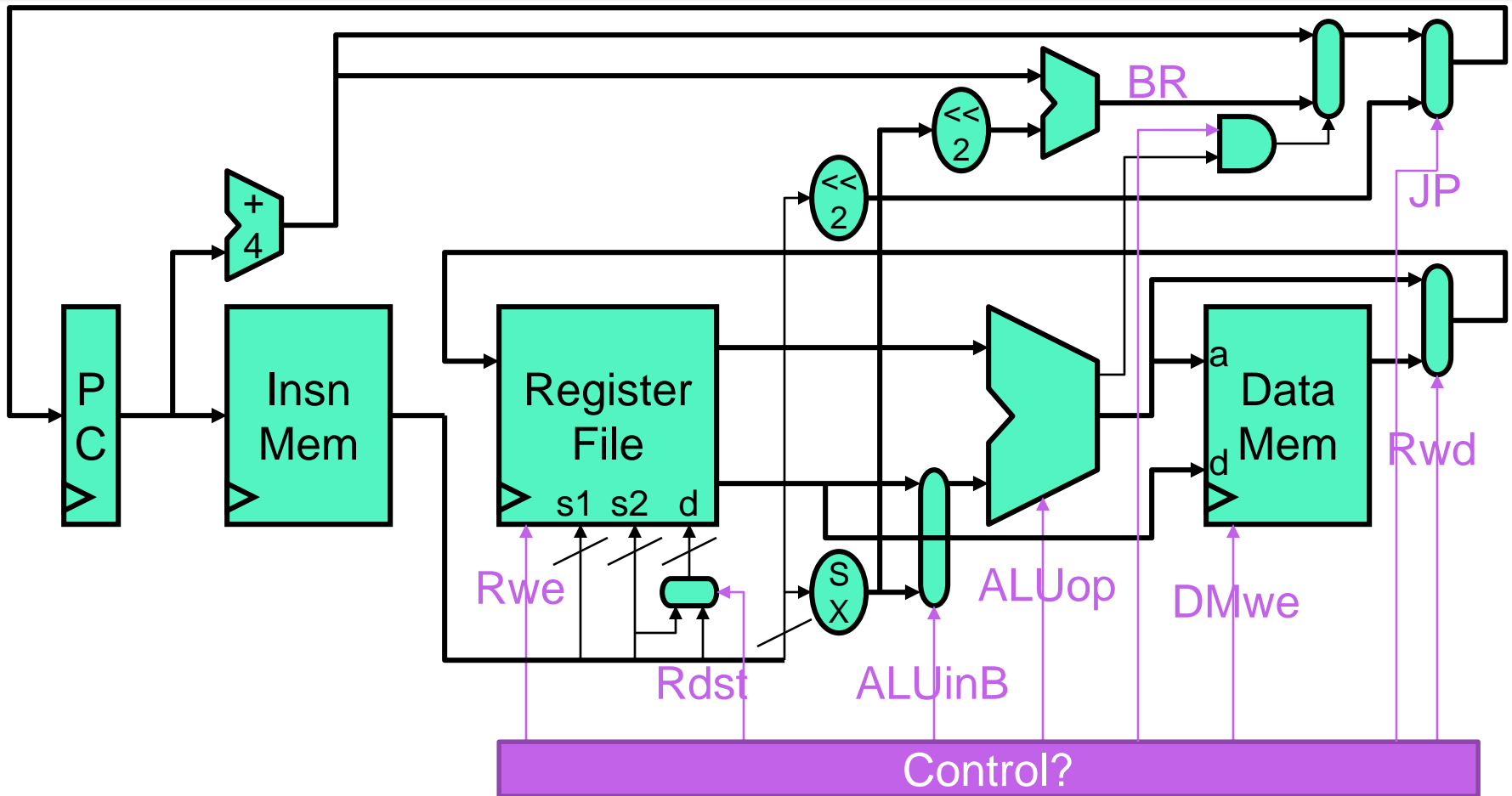

Implementing Control

- Each instruction has a unique set of control signals
 - Most signals are function of opcode
 - Some may be encoded in the instruction itself
 - E.g., the ALUop signal is some portion of the MIPS Func field
 - + Simplifies controller implementation
 - Requires careful ISA design
- Options for implementing control
 1. Use instruction type to look up control signals in a table
 2. Design combinational logic whose outputs are control signals
 - Either way, goal is same: turn instruction into control signals

Control Implementation: ROM

- **ROM (read only memory)**: like a RAM but unwritable
 - Bits in data words are control signals
 - Lines indexed by opcode
- Example: ROM control for our simple datapath

opcode →


	BR	JP	ALUinB	ALUop	DMwe	Rwe	Rdst	Rwd
→ add	0	0	0	0	0	1	1	0
→ addi	0	0	1	0	0	1	0	0
→ lw	0	0	1	0	0	1	0	1
→ sw	0	0	1	0	1	0	0	0
→ beq	1	0	0	1	0	0	0	0
→ j	0	1	0	0	0	0	0	0

ROM vs. Combinational Logic


- A control ROM is fine for 6 insns and 9 control signals
- A real machine has 100+ insns and 300+ control signals
 - Even “RISC”s have lots of instructions
 - 30,000+ control bits (~4KB)
 - Not huge, but hard to make fast
 - Control must be faster than datapath
- Alternative: **combinational logic**
 - It’s that thing we know how to do! *Nice!*
 - Exploits observation: many signals have few 1s or few 0s

Control Implementation Combinational Logic with a Decoder (one-hot representation)

 - Example: combinational logic control for our simple datapath




Datapath and Control Timing

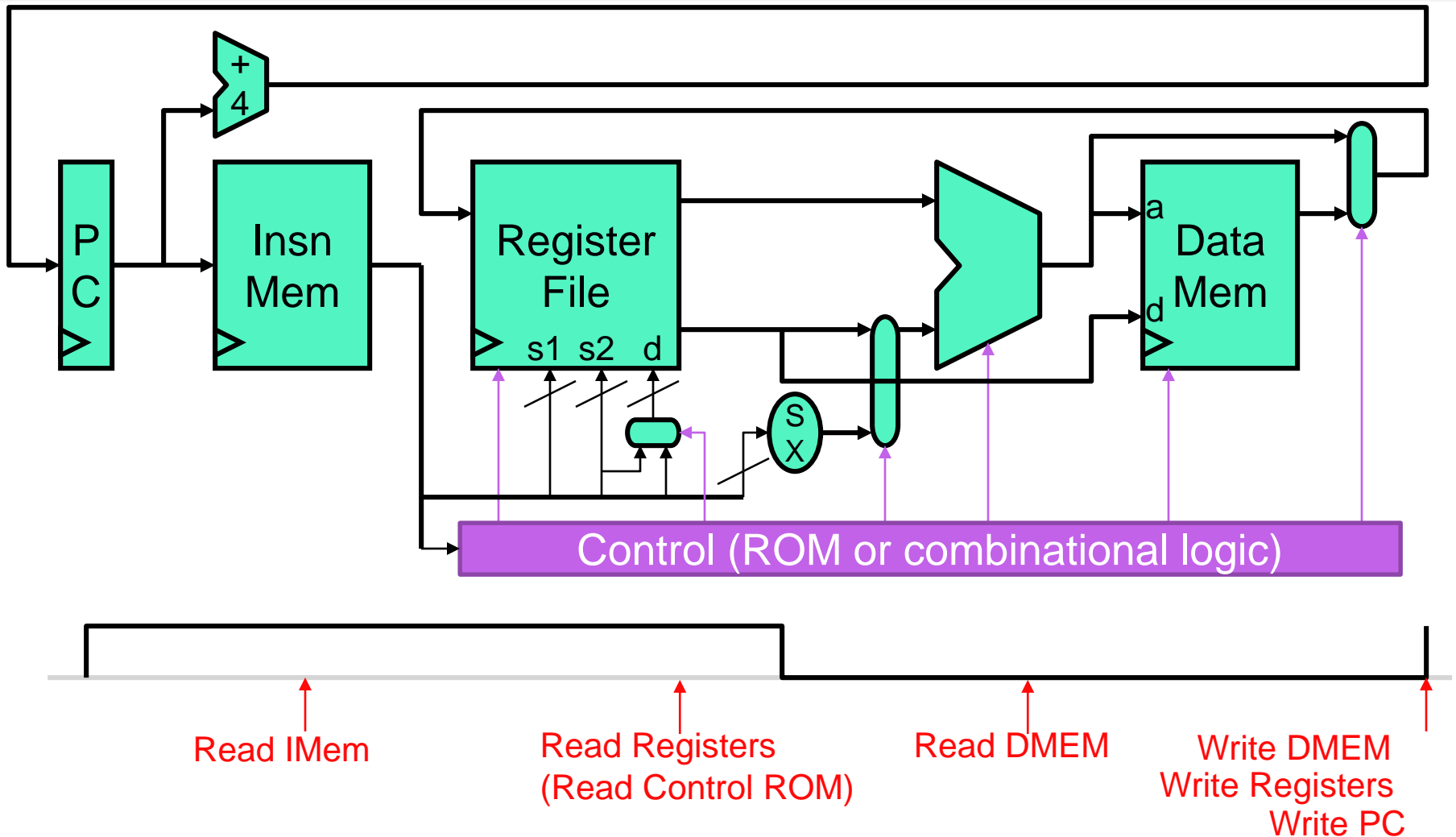

How do we sub-divide timing like this? **Pipelining!** (Covered later)

This Unit: Processor Design

 

- Datapath components and timing
 - Registers and register files
 - Memories (RAMs)
 - Clocking strategies
- Mapping an ISA to a datapath
- Control
- Exceptions

Exceptions

- **Exceptions and interrupts**

- Infrequent (exceptional!) events
 - I/O, divide-by-0, illegal instruction, page fault, protection fault, ctrl-C, ctrl-Z, timer
- Handling requires intervention from operating system
 - End program: divide-by-0, protection fault, illegal insn, ^C
 - Fix and restart program: I/O, page fault, ^Z, timer
- Handling should be transparent to application code
 - Don't want to (can't) constantly check for these using insns
 - Want "Fix and restart" equivalent to "never happened"

Exception Handling

- What does exception handling look like to software?
 - When exception happens...
 - Control transfers to OS at pre-specified exception handler address
 - OS has privileged access to registers user processes do not see
 - These registers hold information about exception
 - Cause of exception (e.g., page fault, arithmetic overflow)
 - Other exception info (e.g., address that caused page fault)
 - PC of application insn to return to after exception is fixed
 - OS uses privileged (and non-privileged) registers to do its “thing”
 - OS returns control to user application
- Same mechanism available programmatically via SYSCALL

MIPS Exception Handling

- MIPS uses registers to hold state during exception handling
 - These registers live on “coprocessor 0”
 - \$14: EPC (holds PC of user program during exception handling)
 - \$13: exception type (SYSCALL, overflow, etc.)
 - \$8: virtual address (that produced page/protection fault)
 - \$12: exception mask (which exceptions trigger OS)
- Exception registers accessed using two **privileged** instructions **mfc0**, **mtc0**
 - Privileged = user process can't execute them
 - mfc0: move (register) from coprocessor 0 (to user reg)
 - mtc0: move (register) to coprocessor 0 (from user reg)
- Privileged instruction **rfe** restores user mode
 - Kernel executes this instruction to restore user program

MIPS Exception Handling


- MIPS uses registers to hold state during exception handling
 - These registers live on “coprocessor 0”
 - \$14: EPC (holds PC of user program during exception handling)
 - \$13: exception type (SYSCALL, overflow, etc.)
 - \$8: virtual address (that produced exception)
 - \$12: exception mask (user mask)
- Exception instructions
 - `sw` (store word) – store them
 - `mfhi` (move from hi) – move from coprocessor 0 (to user reg)
 - `mflo` (move from lo) – move (register) to coprocessor 0 (from user reg)
- Privileged instruction `rfw` restores user mode
 - Kernel executes this instruction to restore user program

DON'T GET TOO OBSESSED ABOUT HOW EXACTLY MIPS DOES THIS – FOCUS ON THE BIG PICTURE AND WHAT MUST HAPPEN IN GENERAL

Implementing Exceptions

- Why do architects care about exceptions?
 - Because we use datapath and control to implement them
 - More precisely... to implement aspects of exception handling
 - Recognition of exceptions
 - Transfer of control to OS
 - Privileged OS mode
- Later in semester, we'll talk more about exceptions (b/c we need them for I/O)

Datapath with Support for Exceptions

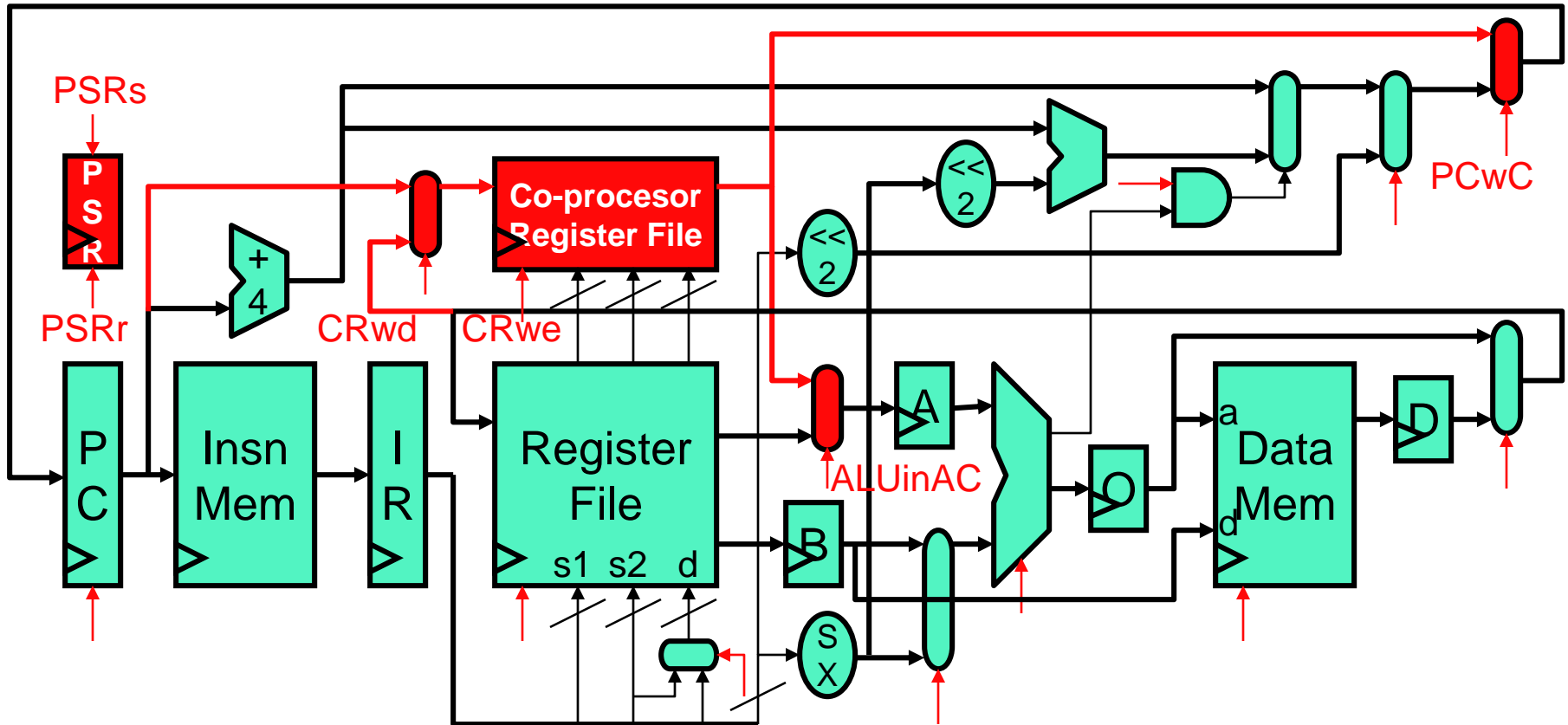

- Co-processor register (CR) file needn't be implemented as RF
 - Independent registers connected directly to pertinent muxes
- **PSR (processor status register):** in privileged mode?


Summary

- We now know how to build a fully functional processor
- But ...
 - We're still treating memory as a black box (actually two green boxes, to be precise)
 - Our fully functional processor is slow. Really, really slow.

“Single-Cycle” Performance

- Useful metric: cycles per instruction (CPI)
- + Easy to calculate for single-cycle processor: $CPI = 1$
 - Seconds/program = (insns/program) * 1 CPI * (N seconds/cycle)
 - ICQ: How many cycles/second in 3.8 GHz processor?
- Slow!
 - Clock period must be elongated to accommodate longest operation
 - In our datapath: lw
 - Goes through five structures in series: insn mem, register file (read), ALU, data mem, register file again (write)
 - No one will buy a machine with a slow clock
 - Not even your grandparents!
 - Biggest issue: data memory itself is sloooooooooooooooooooooooooooooow
- Next up: Speed up data memory!
- Later on: Faster processor cores!

This Unit: Processor Design

 

- Datapath components and timing
 - Registers and register files
 - Memories (RAMs)
 - Clocking strategies
- Mapping an ISA to a datapath
- Control

Next up: Memory Systems