ECE/CS 250 Computer Architecture

Summer 2024

Basics of Logic Design: Storage Elements and the Register File (Sequential Logic)

Tyler Bletsch Duke University

Slides are derived from work by Daniel J. Sorin (Duke), Alvy Lebeck (Duke), and Drew Hilton (Duke)

So far...

- We can make logic to compute "math"
 - Add, subtract ... and you can do mul/div in 350
 - Assume for now that mul/div can be built
 - Bitwise: AND, OR, NOT,...
 - Shifts (left or right)
 - Selection (MUX)
 - ...pretty much anything
- But processors need state (hold value)
 - Registers
 - ...

Storage

- All the circuits we looked at so far are combinational circuits: the output is a Boolean function of the inputs.
- We need circuits that can remember values (registers, memory)
- The output of the circuit is a function of the input <u>and</u> a function of a stored value (state)
- Circuits with storage are called sequential circuits
- Key to storage: feedback loops from outputs to inputs

Ideal Storage – Where We're Headed

• Ultimately, we want something that can hold 1 bit and we want to control when it is re-written



- However, instead of just giving it to you as a magic black box, we're going to first dig a bit into the box
 - I will not test you on the insides of the "flip flop"

Building up to the D Flip-Flop and beyond



(too awkward)

(bad timing)

D Flip-Flop (okay but only one bit) Register

FF Step #1: NOR-based Set-Reset (SR) Latch





R	S	Q
0	0	Q
0	1	1
1	0	0
1	1	

Don't set both S & R to 1. Seriously, don't do it.















SR Latch

- Downside: S and R at once = chaos
- Downside: Bad interface

• So let's build on it to do better

Building up to the D Flip-Flop and beyond



Building up to the D Flip-Flop and beyond



FF Step #2: Data Latch ("D Latch")



Starting with SR Latch



Starting with SR Latch

Change interface to Data + Enable (D + E)

If E=0, then R=S=0. If E=1, then S=D and R=!D









Logic Takes Time

- Logic takes time:
 - Gate delays: delay to switch each gate
 - Wire delays: delay for signal to travel down wire
 - Other factors (not going into them here)
- Need to make sure that signals timing is right
 - Don't want to have races or wacky conditions..

Clocks

- Processors have a clock:
 - Alternates 0 1 0 1
 - Like the processor's internal metronome
 - Latch \rightarrow logic \rightarrow latch in one clock cycle



FF Step #3: Using Level-Triggered D Latches

- First thoughts: Level Triggered
 - Latch enabled when clock is high
 - Hold value when clock is low



- How we'd like this to work
 - Clock is low, all values stable



- How we'd like this to work
 - Clock goes high, latches capture and xmit new val



- How we'd like this to work
 - Signals work their way through logic w/ high clk



- How we'd like this to work
 - Clock goes low before signals reach next latch



- How we'd like this to work
 - Clock goes low before signals reach next latch



- How we'd like this to work
 - Everything stable before clk goes high



- How we'd like this to work
 - Clk goes high again, repeat



- Problem: What if signal reaches latch too early?
 - I.e., while clk is still high



- Problem: What if signal reaches latch too early?
 - Signal goes right through latch, into next stage..



That would be bad...

- Getting into a stage too early is bad
 - Something else is going on there \rightarrow corrupted
 - Also may be a loop with one latch
- Consider incrementing counter (or PC)
 - Too fast: increment twice? Eeek...



Building up to the D Flip-Flop and beyond



FF Step #4: Edge Triggered

- Instead of level triggered
 - Latch a new value at a clock level (high or low)
- We use edge triggered
 - Latch a value at an clock edge (rising or falling)



Our Ultimate Goal: D Flip-Flop



- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables

D Flip-Flop



- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value

D Flip-Flop



- Rising edge triggered D Flip-flop
 - Two D Latches w/ opposite clking of enables
 - On Low Clk, first latch enabled (propagates value)
 - Second not enabled, maintains value
 - On High Clk, second latch enabled
 - First latch not enabled, maintains value

D Flip-Flop



- No possibility of "races" anymore
 - Even if I put 2 DFFs back-to-back...
 - By the time signal gets through 2nd latch of 1st DFF 1st latch of 2nd DFF is disabled
- Still must ensure signals reach DFF before clk rises
 - Important concern in logic design "making timing"

D Flip-flops (continued...)

- Could also do falling edge triggered
 - Switch which latch has NOT on clk

- D Flip-flop is ubiquitous
 - Typically people just say "latch" and mean DFF
 - Which edge: doesn't matter
 - As long as consistent in entire design
 - We'll use rising edge

D flip flops

- Generally don't draw clk input
 - Have one global clk, assume it goes there
 - Often see > as symbol meaning clk
- Maybe have explicit enable
 - Might not want to write every cycle
 - If no enable signal shown, implies always enabled
 - Inside DFF, E signal is ANDed with Clk: if E is off, Clk is ignored (so we don't commit changes)



Get output and NOT(output) for "free"

D	Q
	DFF
>	Q

Skipping ahead to the D Flip-flop

- There's the **Data** input what to be saved
- There's a clock: a regular oscillation between 0 and 1 that tells us *when* to save a value; it's edge triggered
 - Configured to store at every rising edge (default) or every falling edge
 - Generally drawn as a > notch in the component; may be omitted in schematics (a single global clock is implied)



- There may be an **Enable** line: clock edges that occur when disabled don't "count". (If omitted, then always enabled)
- Stored data comes out on the Q line
 - Also get its negation on the **!Q** line for free



Building up to the D Flip-Flop and beyond



Stick a bunch of DFFs together to make a register

- Make an *n*-bit register? Combine *n* DFFs together!
 - A MIPS register can be made with 32 flip flops



Next evolution: multiple registers





Multiple registers: Register File

- So do we just replicate this 32 times to get the 32 registers for a MIPS processor?
 - Not exactly
- Register File (the physical storage for the regs)
 - MIPS register file has 32 32-bit registers
- How do we build a Register File using D Flip-Flops?
- What other components do we need?

Register File Design



First: A Decoder

- First task: convert binary number to "one hot"
 - N bits in
 - 2^{N} bits out
 - 2^{N-1} bits are 0, 1 bit (matching the input) is 1



Decoder Logic

- Decoder basically AND gates for each output:
 - Out₀ only on if input 000



In practice >4 converted to multiple gates

Decoder Logic

• Decoder basically AND gates for each output:





Repeat for all outputs: AND together right bits (gets messy fast on a slide)

Register File

- Now we know how to **write**:
 - Send write data to all regs
 - Use decoder to convert reg # to one hot
 - Use one hot encoding of reg # to enable right reg
- Still need to fix read side
 - 32 input mux (the way we've made it) not realistic
 - To do this: expand our world from $\{1,0\}$ to $\{1, 0, Z\}$



- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - This wire is 0 (it has no water)



- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - This wire is 1 (it is full of water)



- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose a gate drives a 0 onto this wire
 - Think of it as sucking the water out



- To understand Z, let's make an analogy
 - Think of a wire as a pipe
 - Has water = 1
 - Has water = 0
 - Suppose the gate now drives a 1
 - Think of it as pumping water in



Remember this rule?

• Remember I told you not to connect two outputs?



- If one gate tries to drive a 1 and the other drives a 0
 - One pumps water in.. The other sucks it out
 - Except it's electric charge, not water
 - "Short circuit" \rightarrow lots of current \rightarrow lots of heat

So this third option: Z

- There is a third possibility: Z ("high impedance")
 - Neither pushing water in, nor sucking it out
 - Just closed off/blocked
 - Prevents electricity from flowing through
- Gate that gives us Z : Tri-state





We've had this rule one day... and you break it

It's ok to connect multiple outputs together Under one circumstance:

All but one must be outputting Z at any time



Mux, implemented with tri-states



Register File

Now we can write and read in one clock cycle!



Ports

- What we just saw: read port
 - Ability to do one read / clock cycle
 - May want more: read 2 source registers per instr
 - Maybe even more if we do many instrs at once
 - This design: can just replicate port
 - Another decoder
 - Another set of tri-states
 - Another output bus (wire connecting the tri-states)
- Earlier: write port
 - Ability to do one write/cycle
 - Could add more

Minor Detail

- FYI: This is not how a modern register file is implemented
 - (Though it is how other things are implemented)
 - Actually done with SRAM
 - We'll see that later this semester...

Summary

Can layout logic to compute things Add, subtract,... Now can store things D flip-flops Registers Also understand clocks

Just about ready to make a datapath!